

CS / EE 320
Computer Organization and
Assembly Language
Spring 2025
Lecture 17


Shahid Masud

Topics: From Single Cycle MIPS to Multicycle MIPS, Pipelining


- Timing calculations in Single-Cycle Simple MIPS CPU
- How to add pipelining in simple MIPS CPU
- Detailed analysis of 5-Stage Pipelined MIPS CPU
- Calculations Throughput, Latency, Critical Path of 5-Stage MIPS CPU
- Design of individual Pipelined stages in a 5-Stage MIPS CPU
- Hazards in Pipelined MIPS CIPS
 - Structural Hazard (Hardware Related)
 - Data Hazard (Due to Assembly program)
 - Control Hazard (Architecture related)

SIMPLE MIPS WITH NO PIPELINE

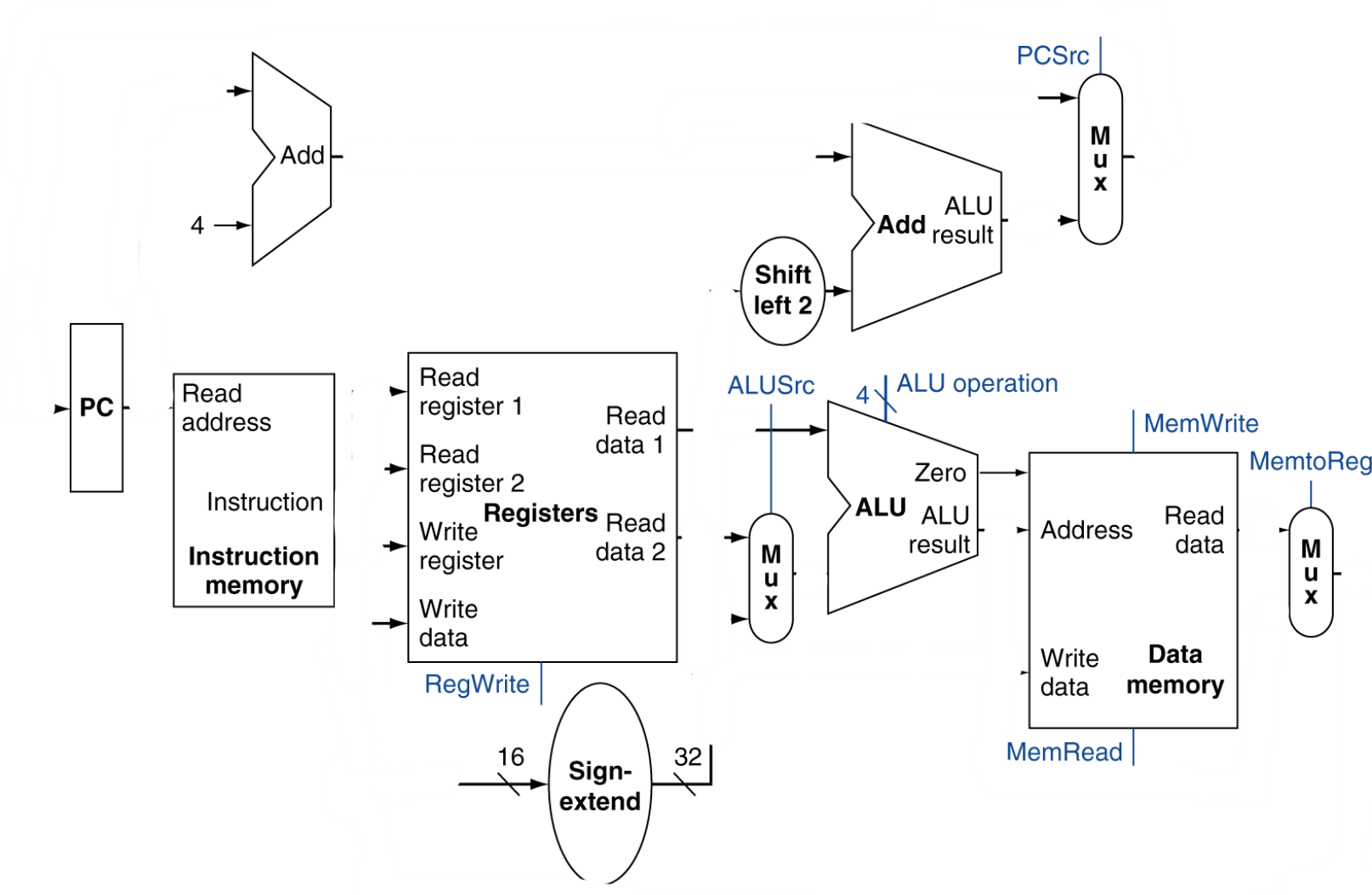
Full Datapath – for practice of connections



Full Datapath

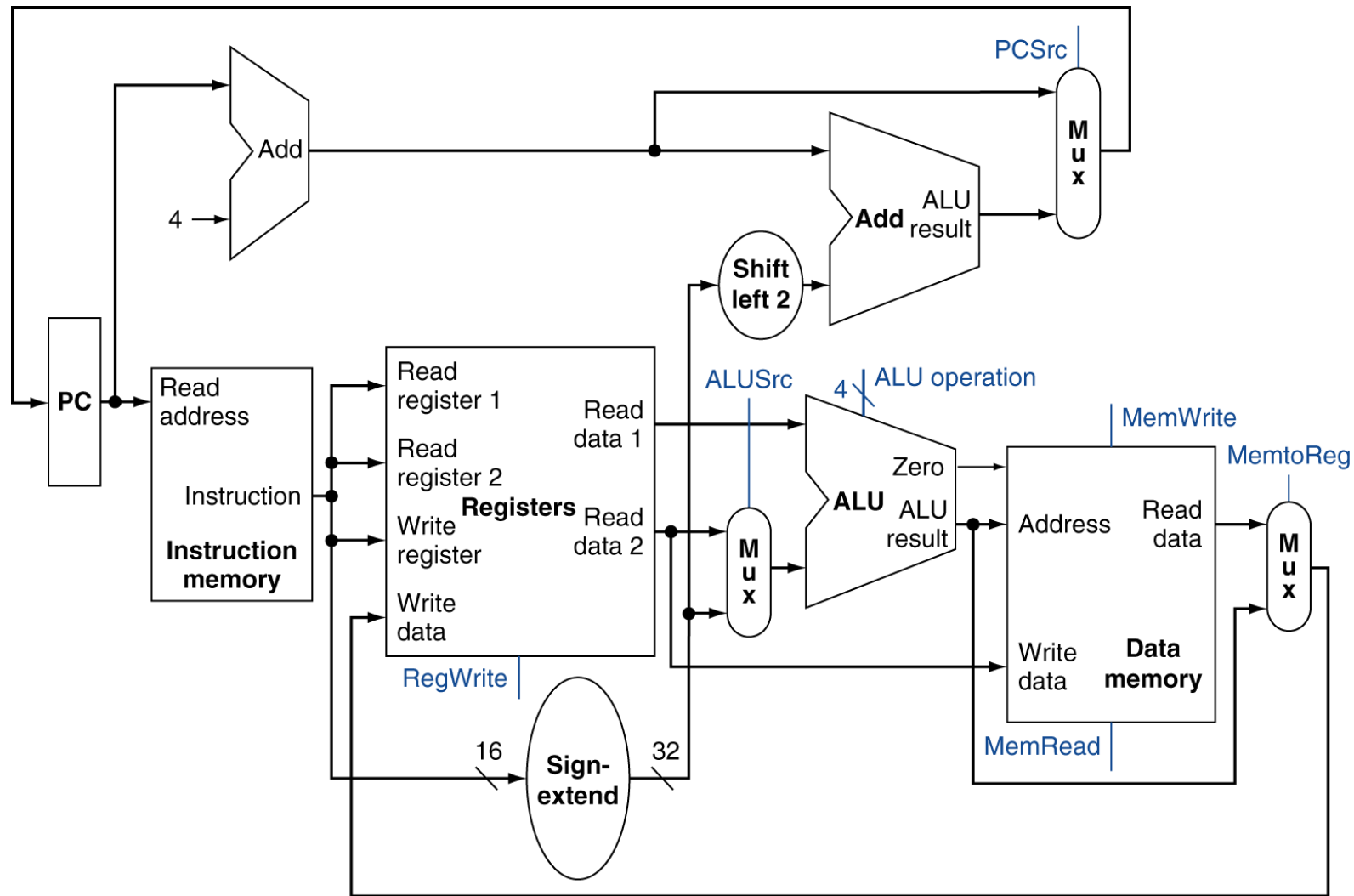


MIPS Datapath With Control

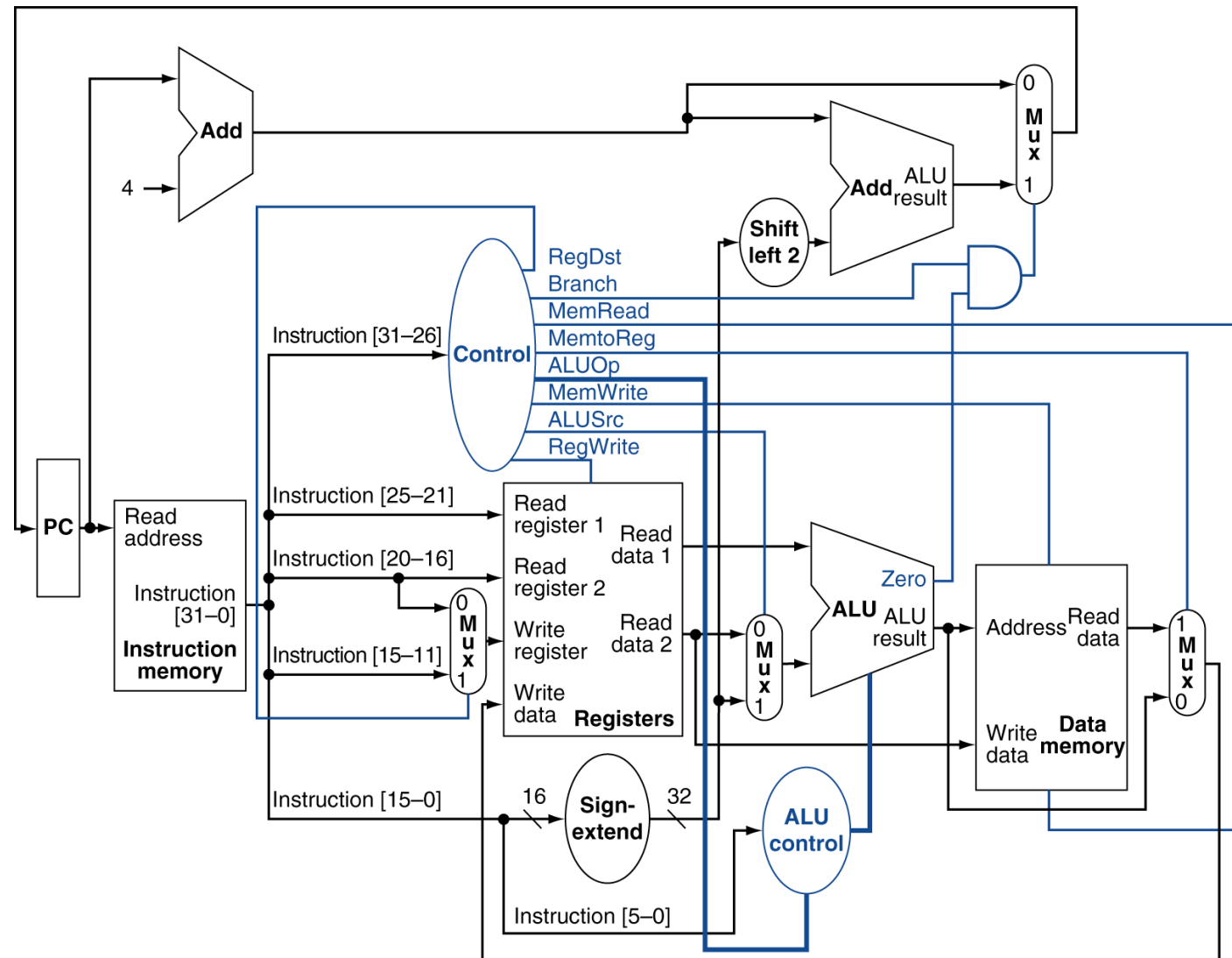


BASICS OF PIPELINING

What Is Pipelining?

 - Laundry Example
- Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, and fold
- Washer takes 30 minutes
- Dryer takes 40 minutes
- “Folding” takes 20 minutes
- One load takes 90 minutes




What Is Pipelining? ...contd

 

Sequential laundry takes 6 hours for 4 loads

If they learned pipelining, how long would laundry take?

Overlapping Different Operations

 


- Pipelining doesn't help latency of single task, it helps throughput of entire workload
- Pipeline rate limited by slowest pipeline stage
- Multiple tasks operating simultaneously
- Potential speedup = Number pipe stages
- Unbalanced lengths of pipe stages reduces speedup
- Time to "fill" pipeline and time to "drain" it reduces speedup

Introducing Pipelining for MIPS

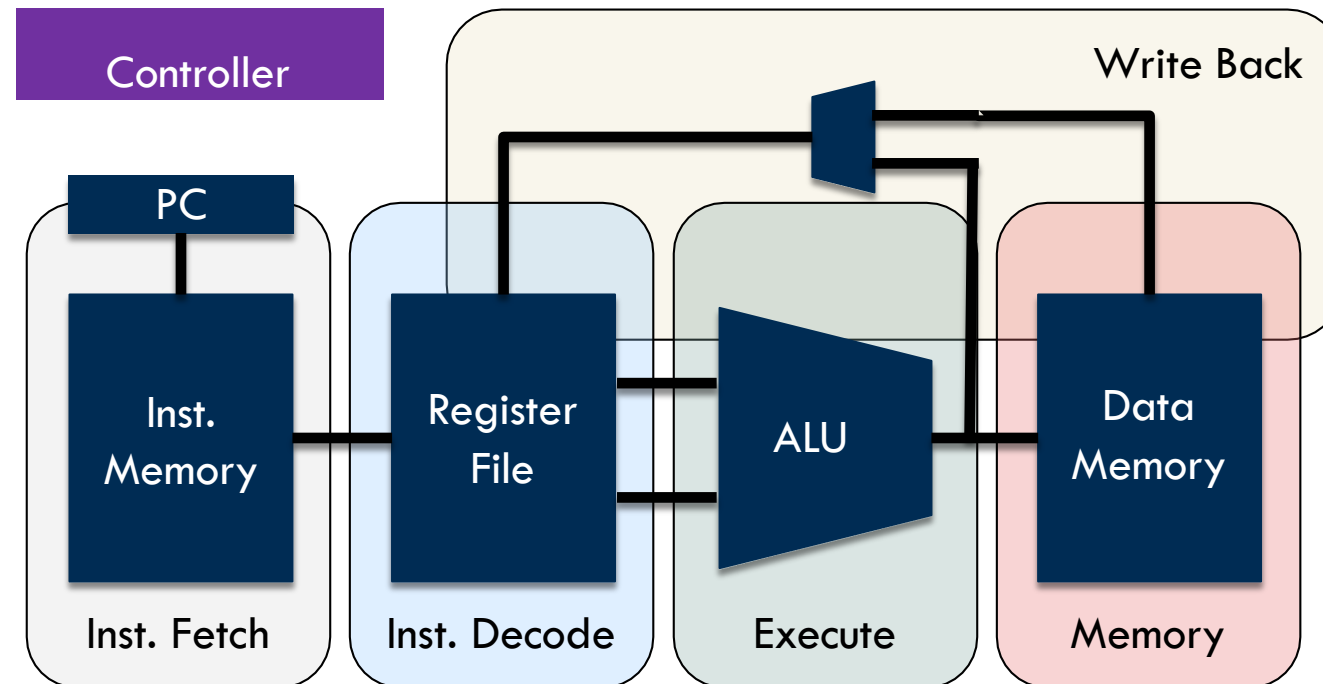
Example: simple MIPS architecture

Critical path includes all of the processing steps



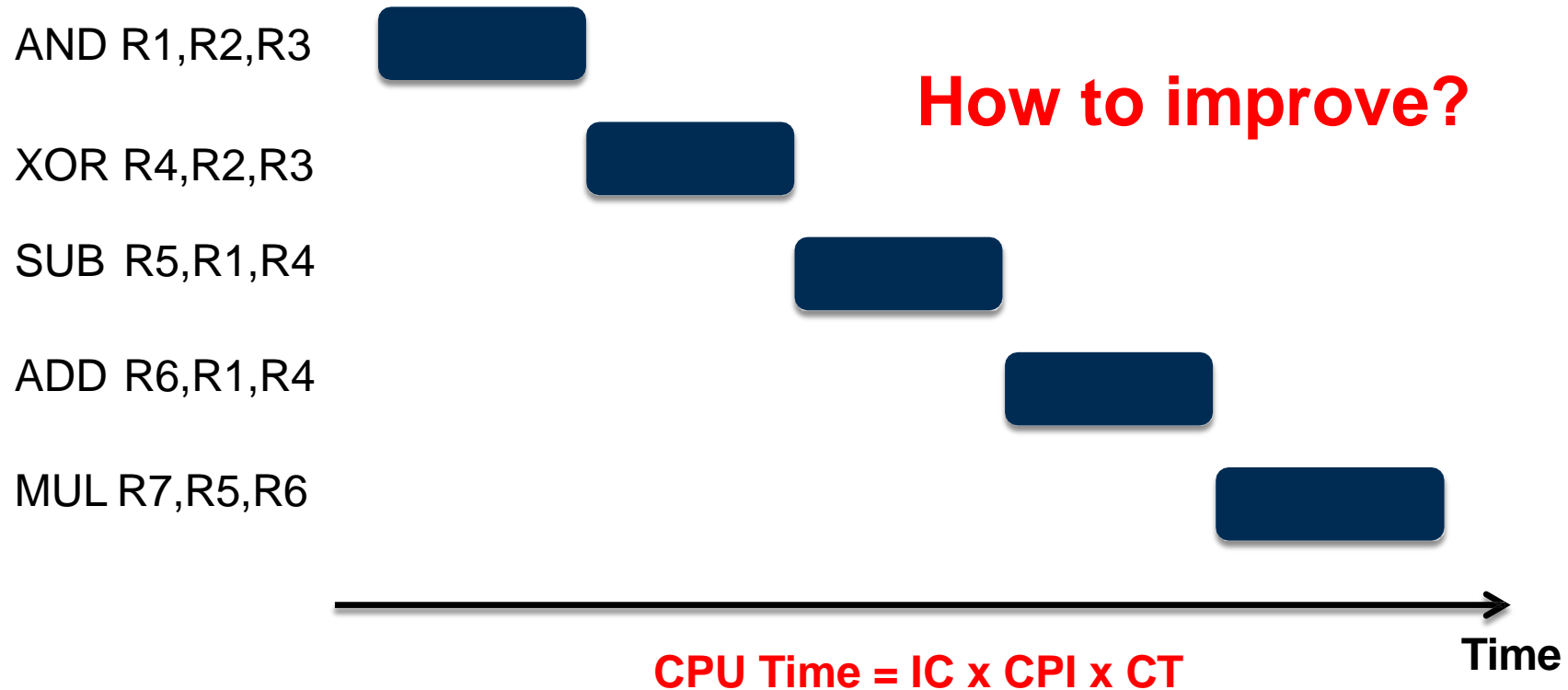Example program


CT=6ns; CPU Time = $5 \times 1 \times 6\text{ns} = 30\text{ns}$



RISC Instruction Set

- Every instruction can be implemented in at most 5 clock cycles/stages
 - ◆ Instruction fetch cycle (IF): send PC to memory, fetch the current instruction from memory, and update PC to the next sequential PC by adding 4 to the PC.
 - ◆ Instruction decode/register fetch cycle (ID): decode the instruction, read the registers corresponding to register source specifiers from the register file.
 - ◆ Execution/effective address cycle (EX): perform Memory address calculation for Load/Store, Register-Register ALU instruction and Register-Immediate ALU instruction.
 - ◆ Memory access (MEM): Perform memory access for load/store instructions.
 - ◆ Write-back cycle (WB): Write back results to the dest operands for Register-Register ALU instruction or Load instruction.

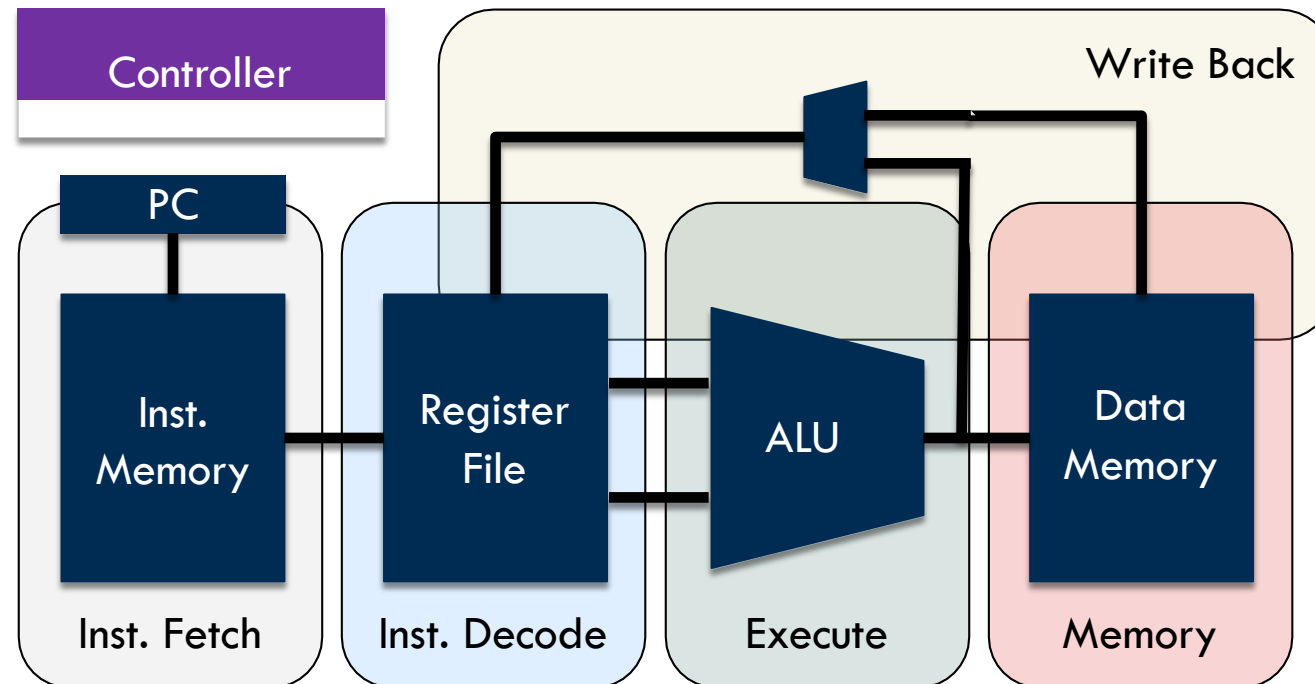Each processing step finishes in a fraction of a cycle
Idle resources can be reused for processing next
instruction




Non-Pipeline Architecture



Example program

CT=1.5ns; CPU Time = $5 \times 5 \times 1.5\text{ns} = 37.5\text{ns} > 30\text{ns}$


WORSE!!

 

Developing a Multi-cycle Data Path


Develop Simple Five-Stage MIPS Pipeline

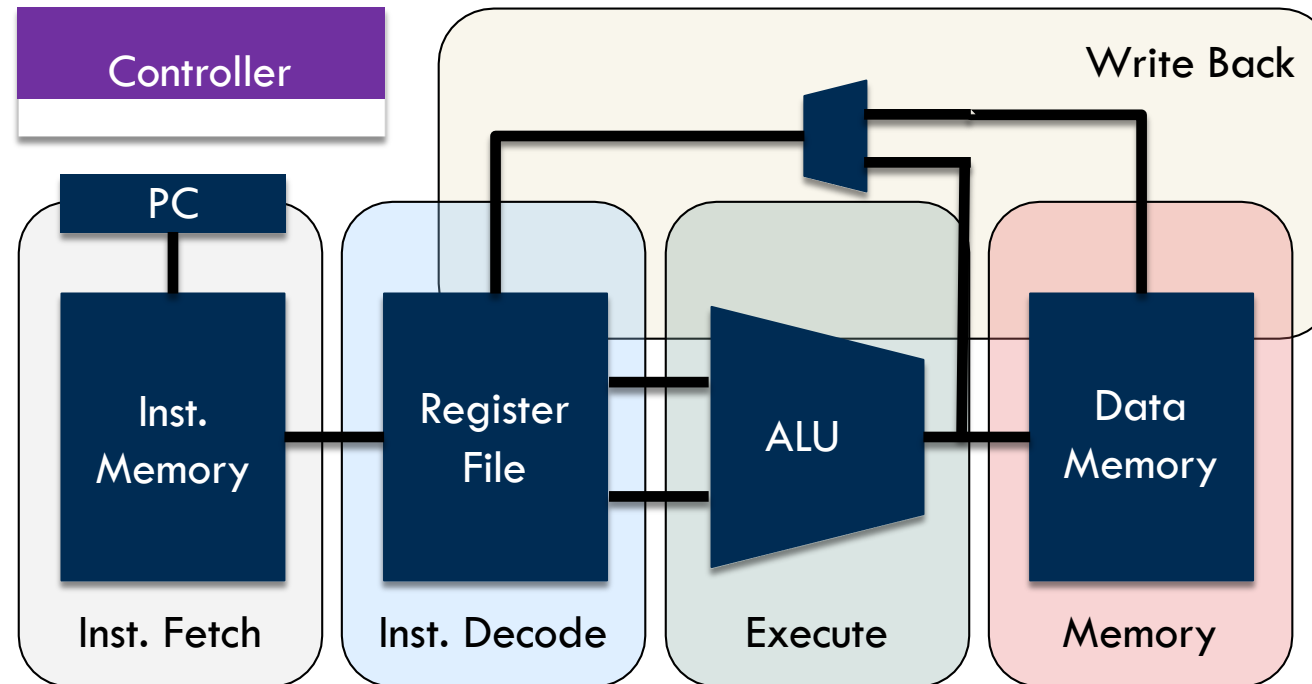A pipelined load-store architecture that processes up to one instruction per cycle




Five stage pipeline

Critical path determines the cycle time

 

Identify CPU Operations where
Pipeline Registers could be Inserted



Recap - Full Datapath

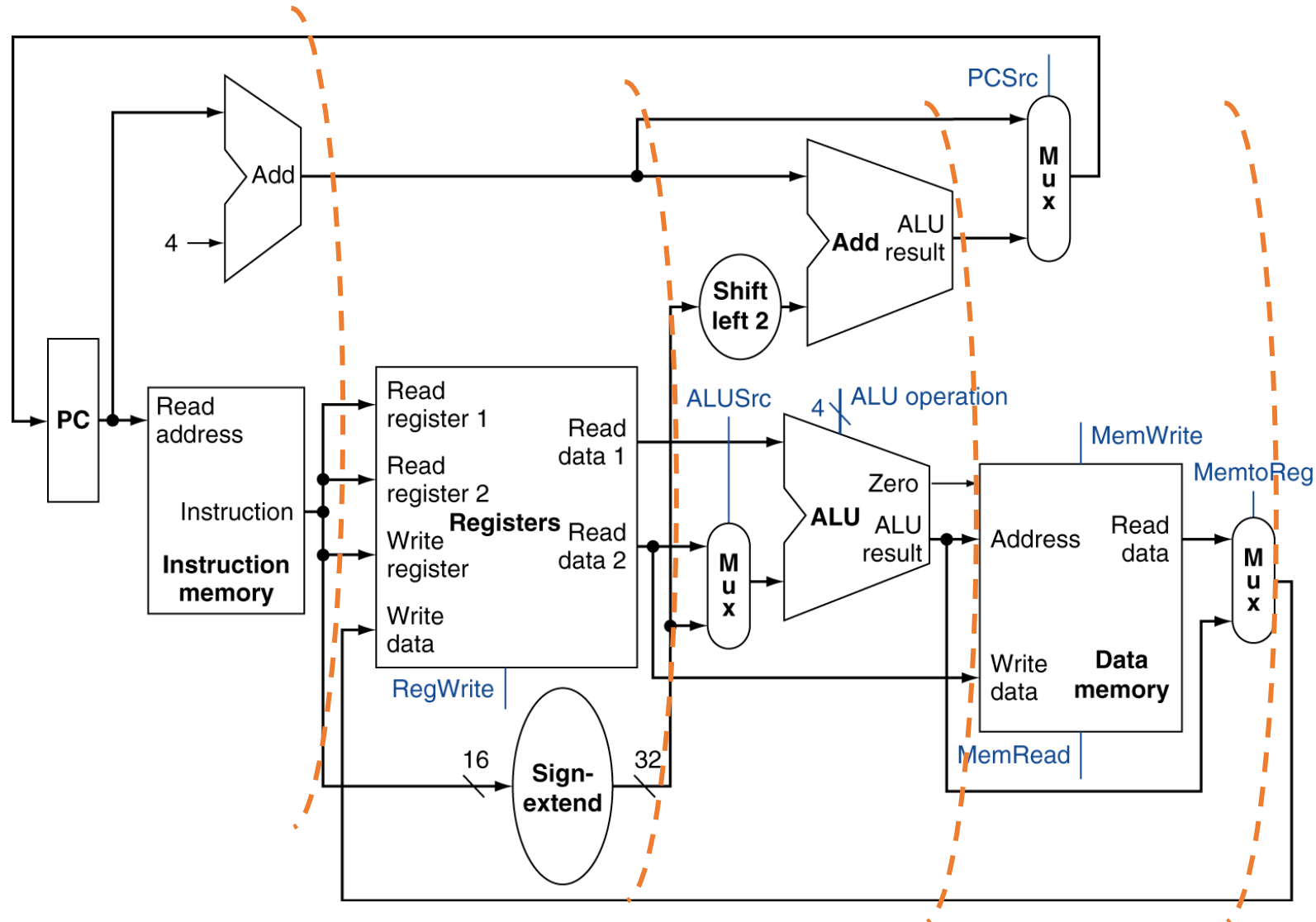

- Read an instruction from memory (I-Memory)
 - Use the program counter (PC) to index into the I- Memory
 - Compute New PC (NPC) by incrementing current PC
 - What about branches?
 - (later?)



- Update pipeline registers
 - Write the instruction into the pipeline registers

Instruction Fetch Stage

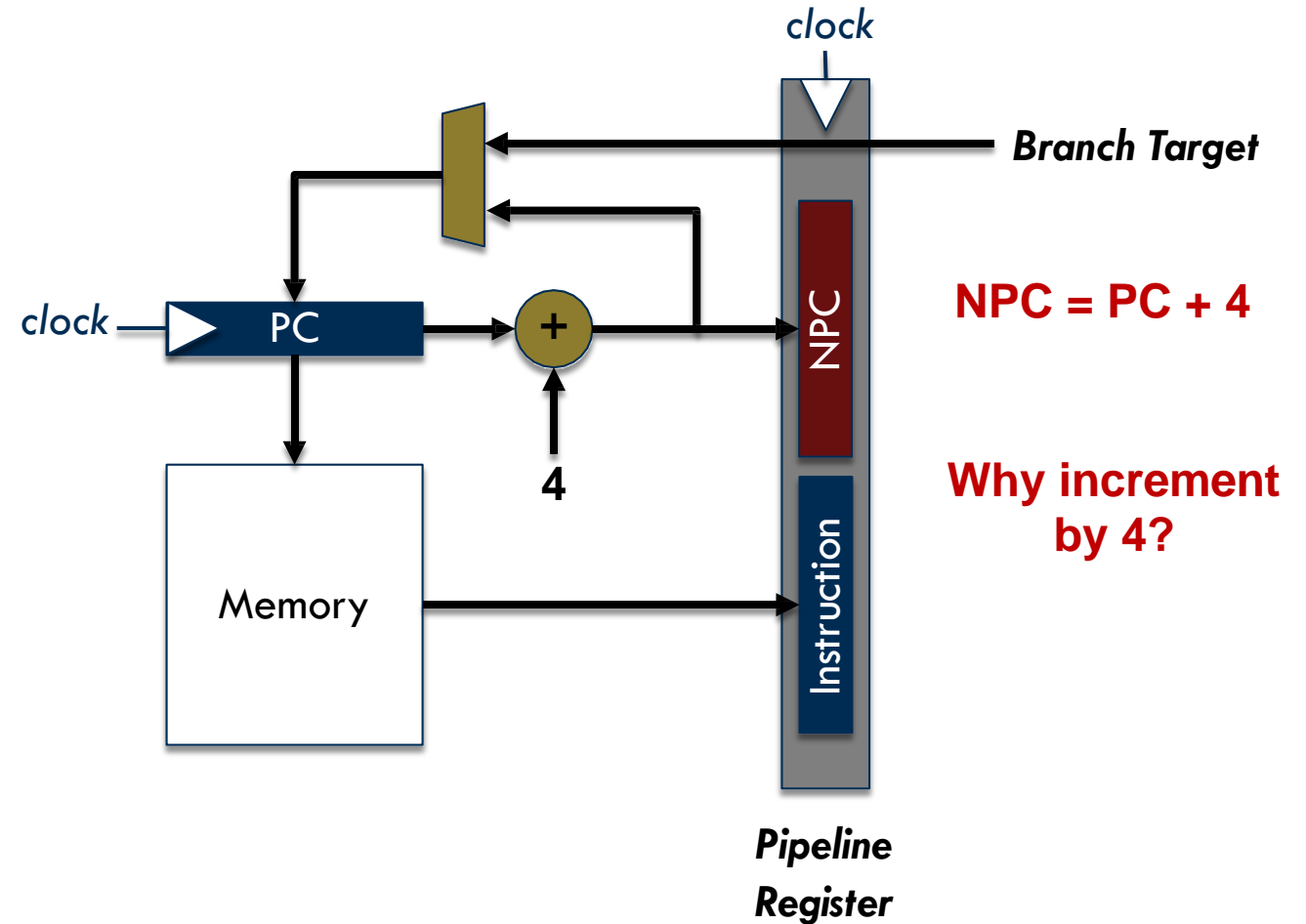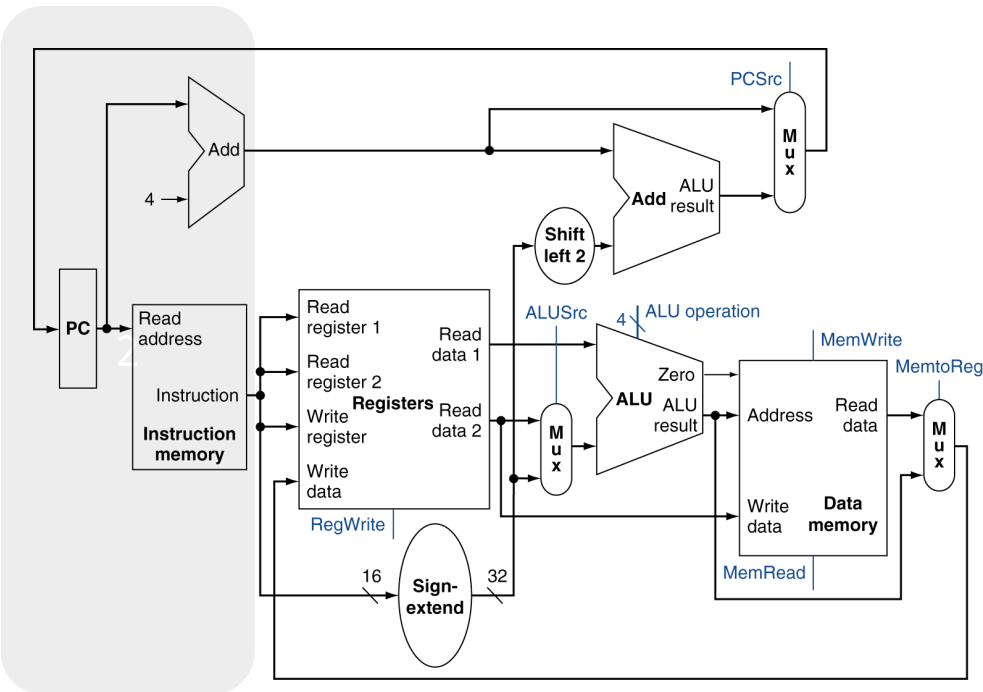

- ▮ Generate control signals for the opcode bits
- ▮ Read source operands from the register file (RF)
 - Use the specifiers for indexing RF
 - How many read ports are required?
- ▮ Update pipeline registers
 - Send the operand and immediate values to next stage
 - Pass control signals and NPC to next stage

Instruction Decode Stage

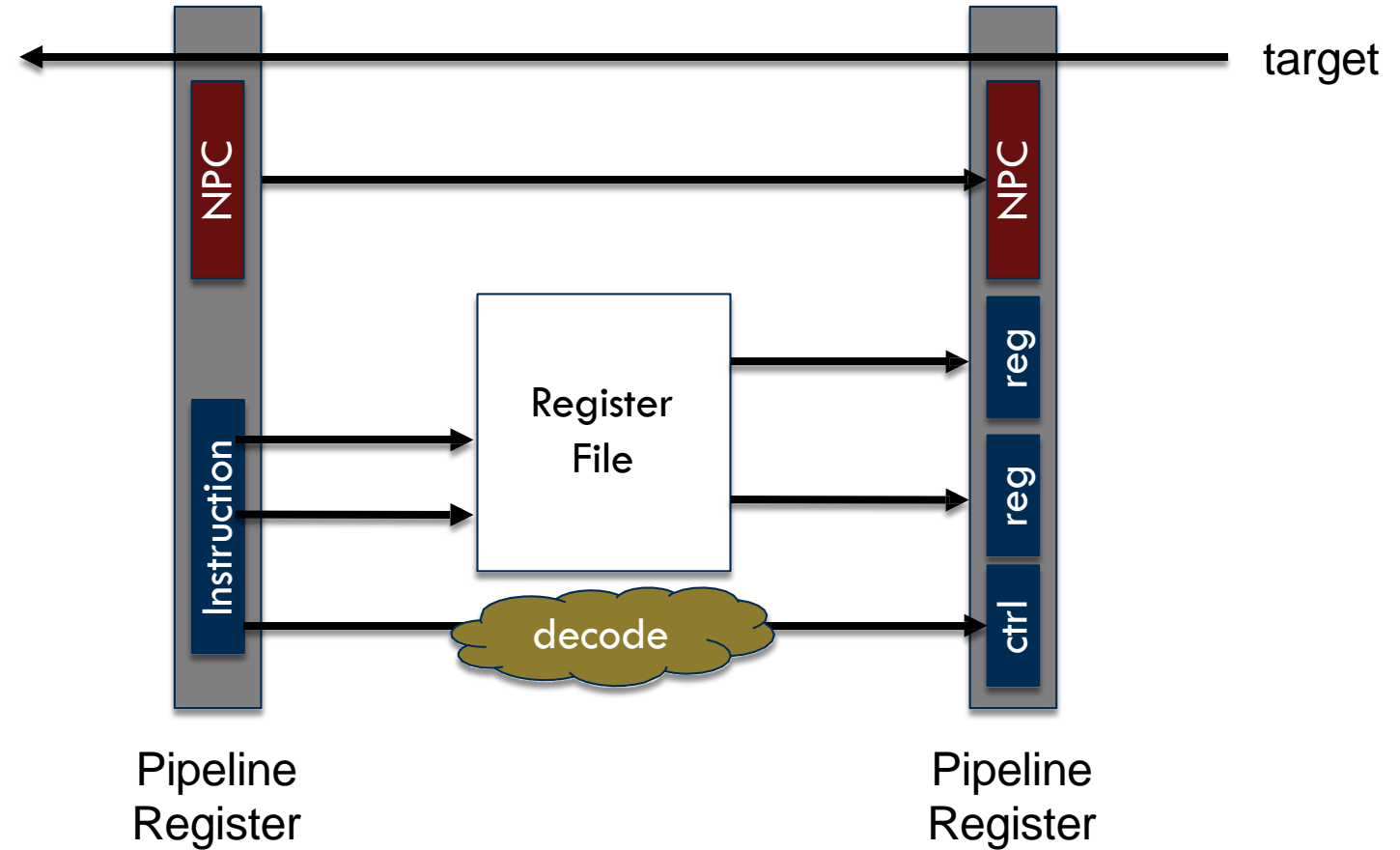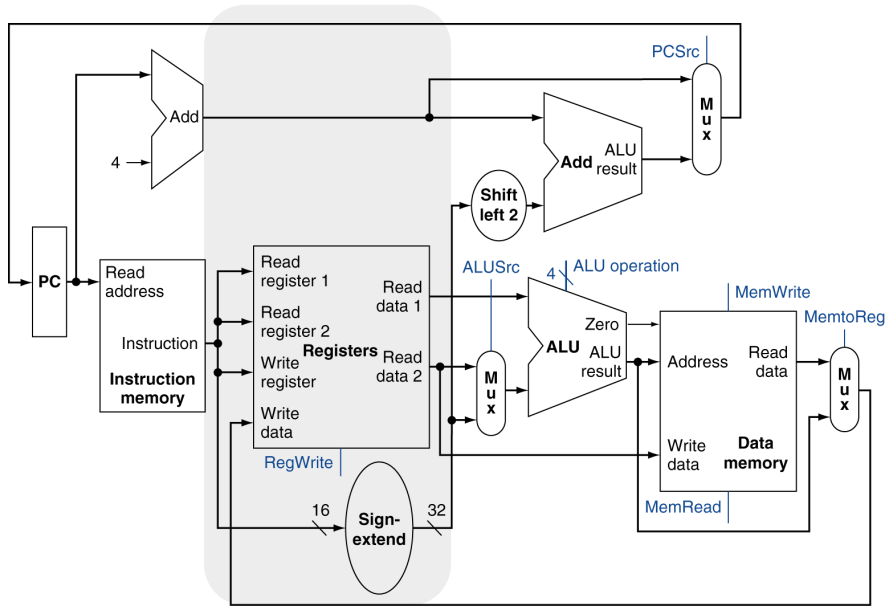

▮ Perform ALU operation

Compute the result of ALU

- Operation type: control signals
- First operand: contents of a register
- Second operand: either a register or the immediate value



Compute branch target

- $\text{Target} = \text{NPC} + \text{immediate}$

▮ Update pipeline registers

Control signals, branch target, ALU results, and destination

Instruction Execute Stage

 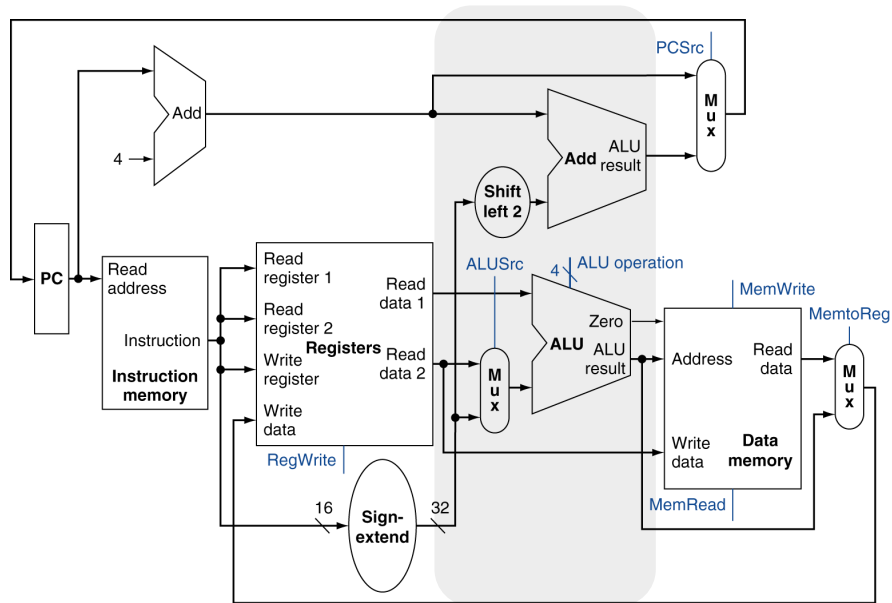

Access data memory

- Load/store address: ALU outcome

- Control signals determine read or write access



Update pipeline registers

- ALU results from execute

- Loaded data from D-Memory

- Destination register

Memory Access Stage

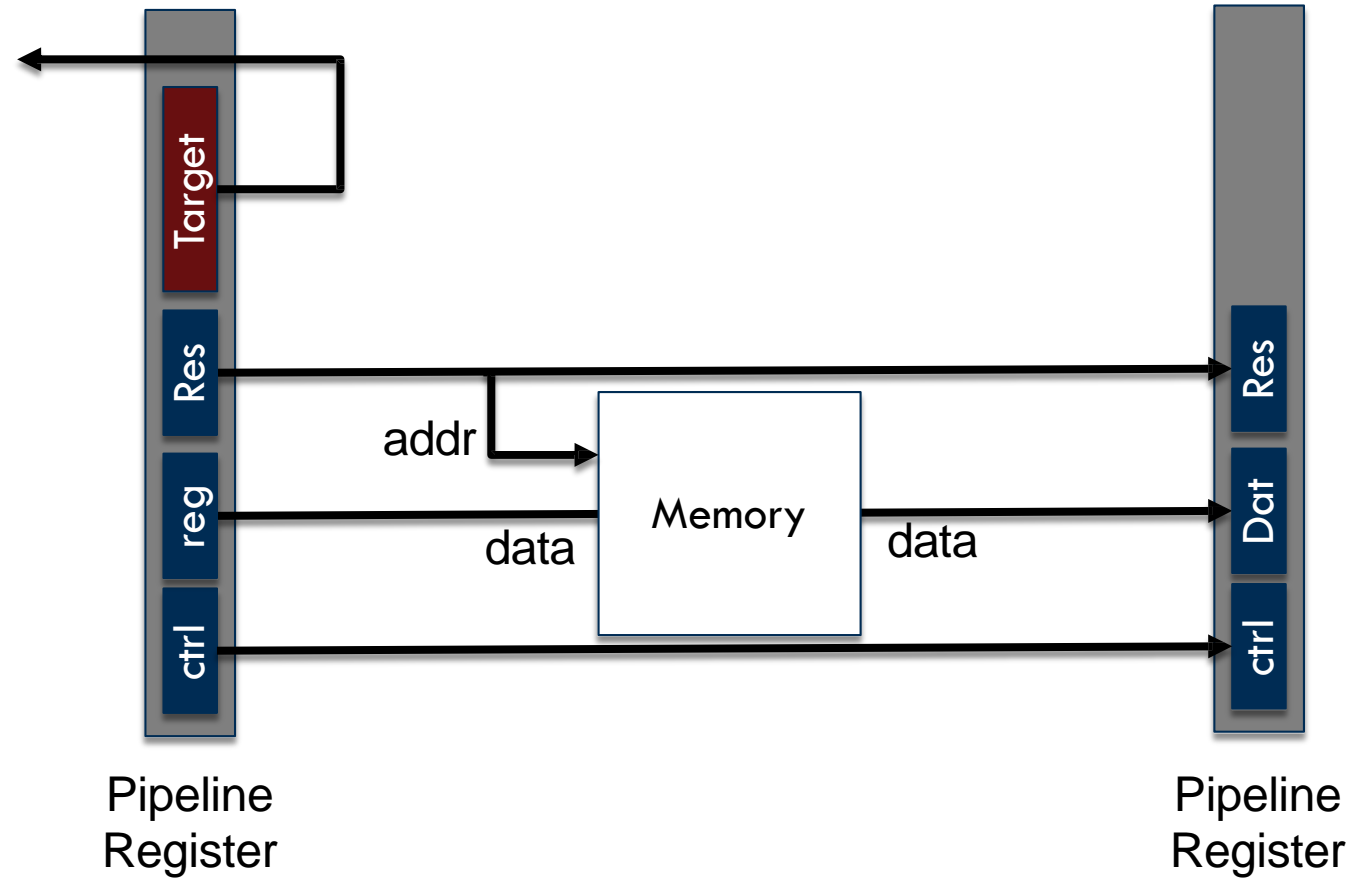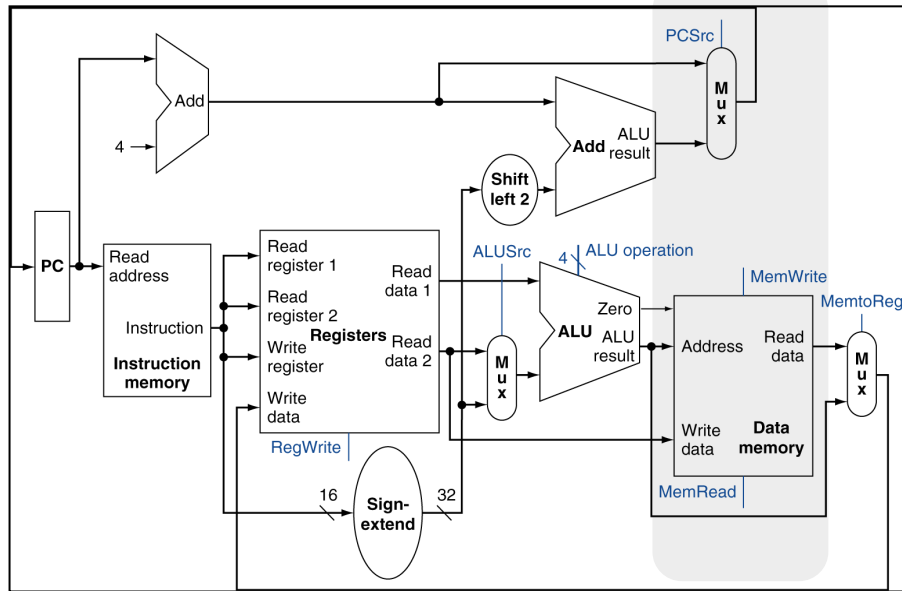

Update register file


Control signals determine if a register write is needed

Only one write port is required

- Write the ALU result to the destination register, or
- Write the loaded data into the register file

Complete Five Stages of Pipeline

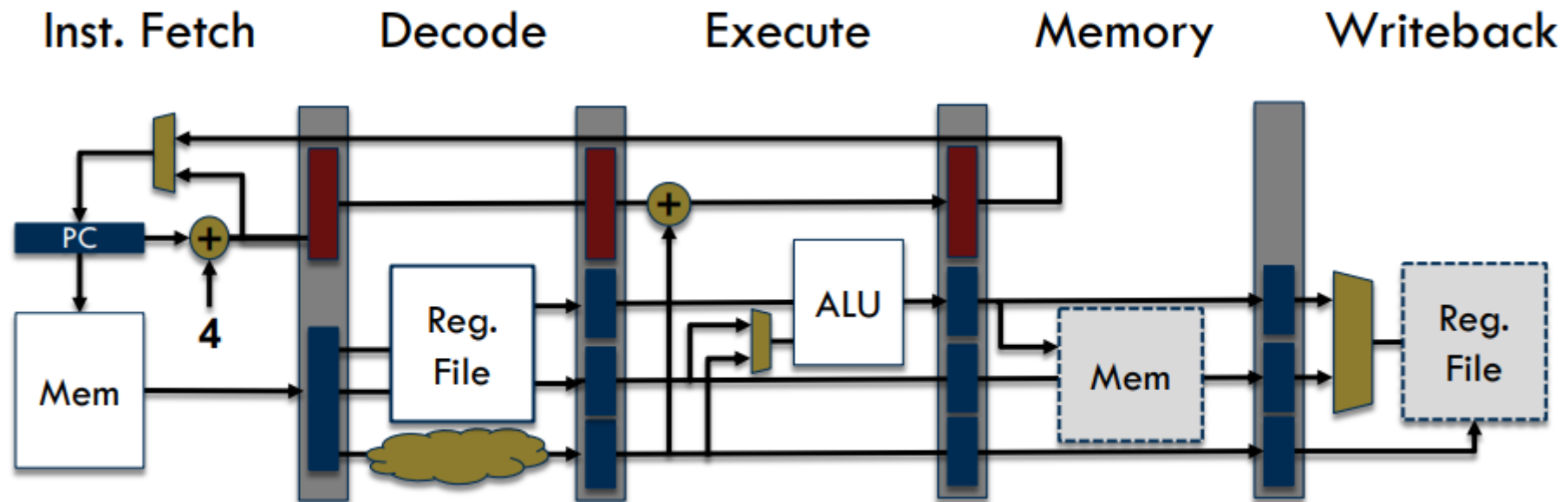- Is there enough resources to keep the pipeline stages busy all the time?




Improving Resource Utilization


Efficient MIPS CPU Design

- Can we eliminate two adders?
- How to share (or reuse) a resource (say ALU) in different clock cycles?
- Store results in registers.
- Of course, more multiplexing may be required!
- Resources in this design: RF, ALU, MEM.


Single Cycle Datapath

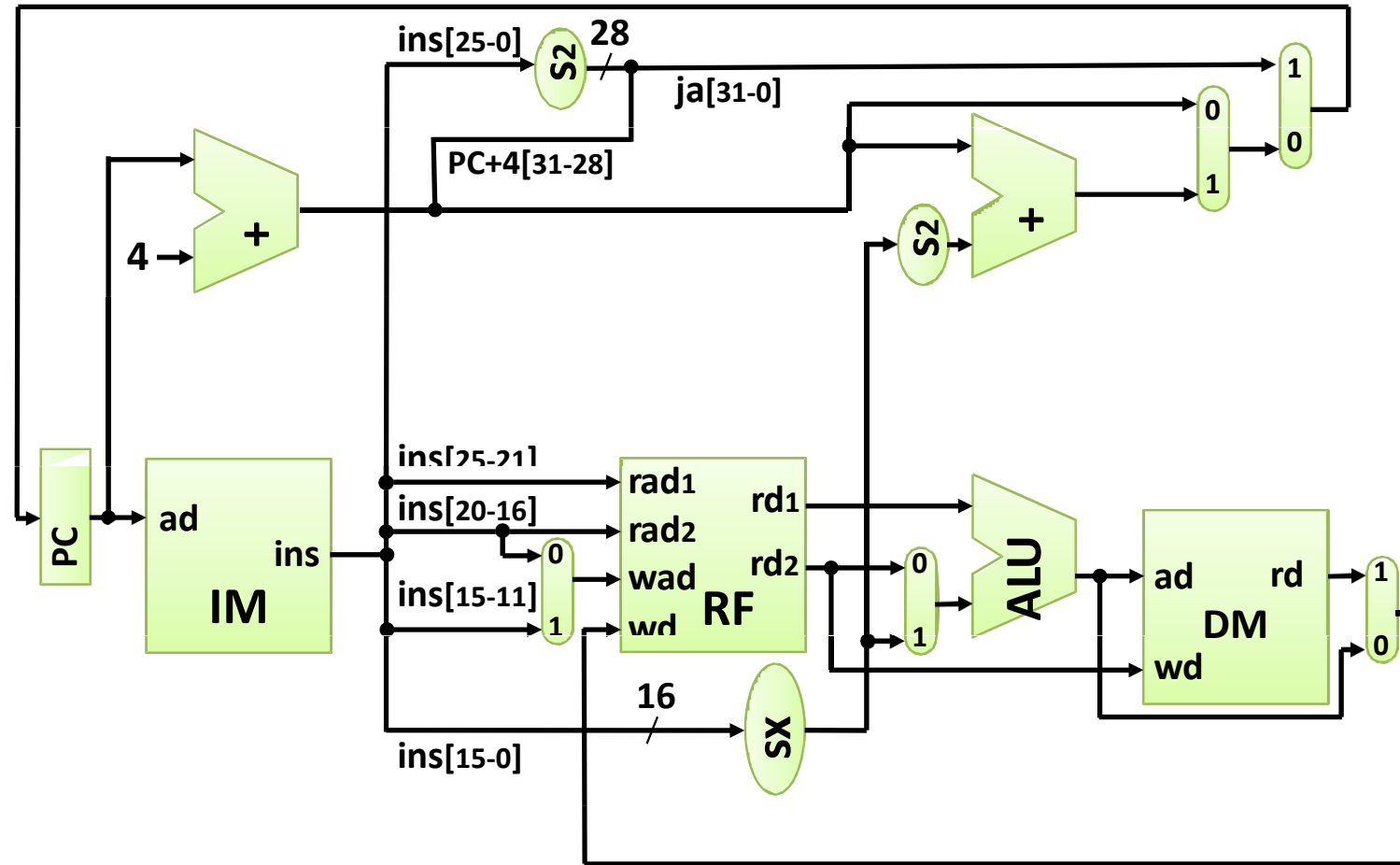


Merge IM and DM, Rearrange Diagram

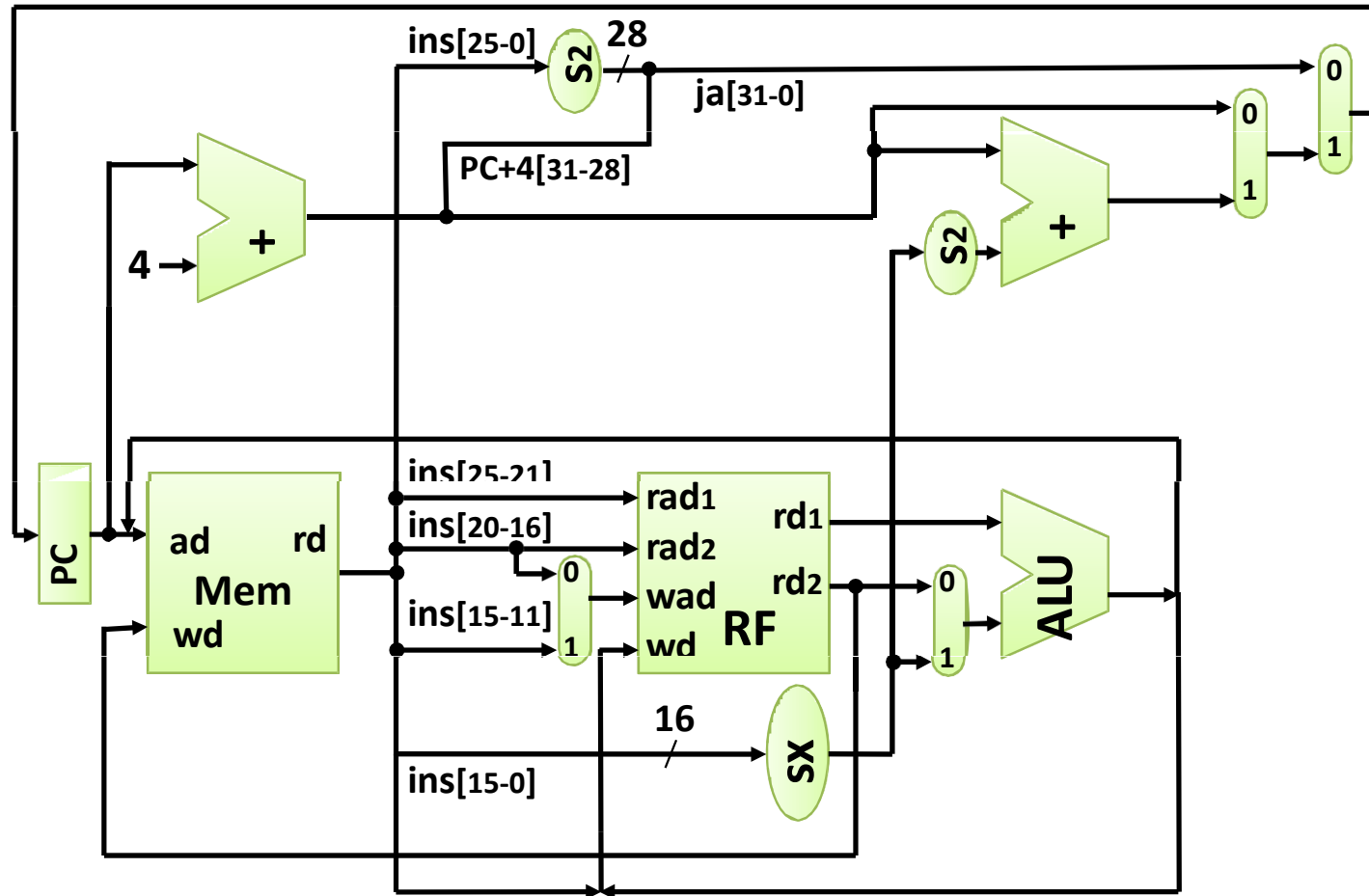


Combine Adders - Rearrange Diagram

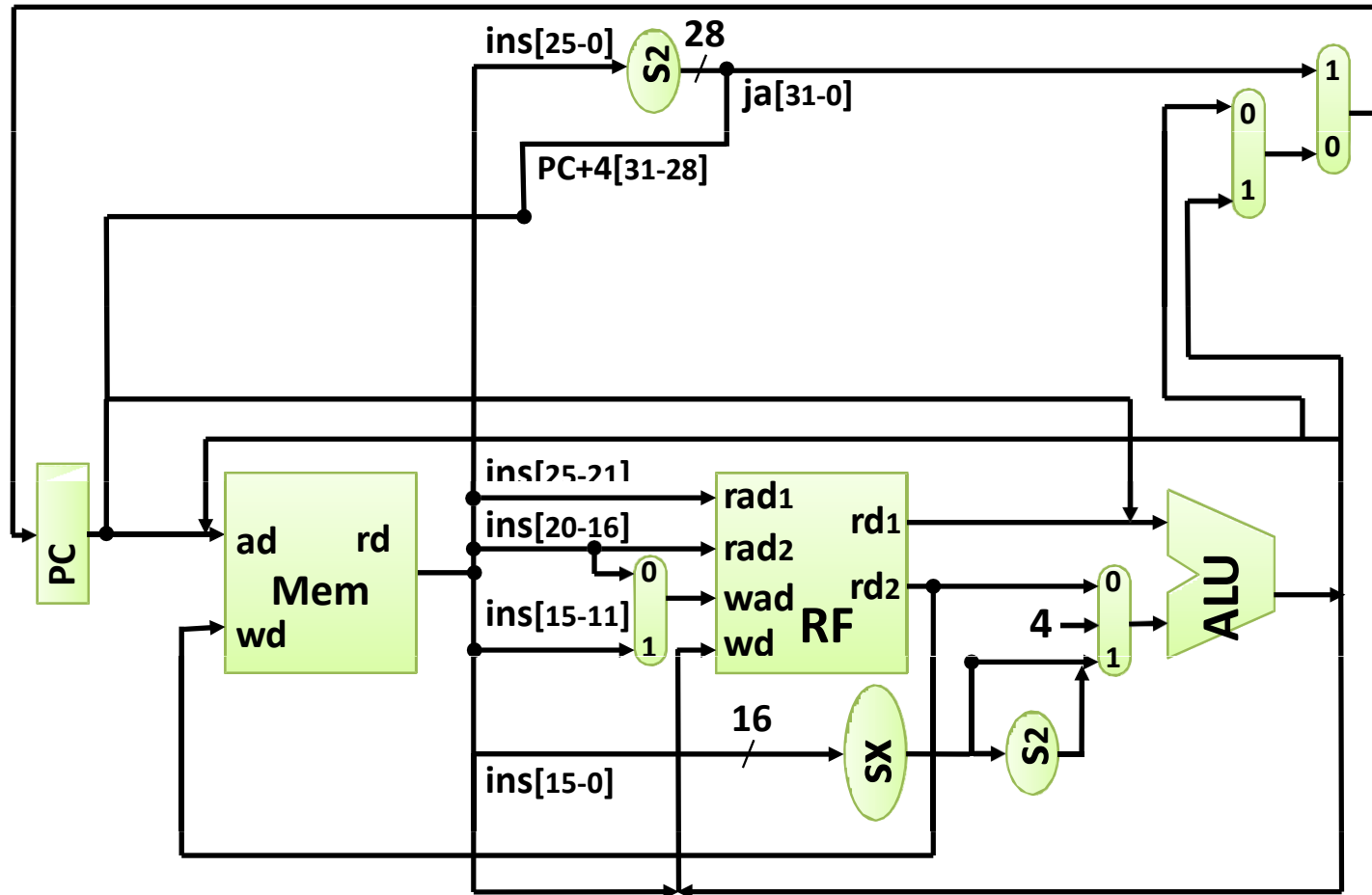


Introduce registers

 

 
Introduce ALU Multiplexers at Input and Output



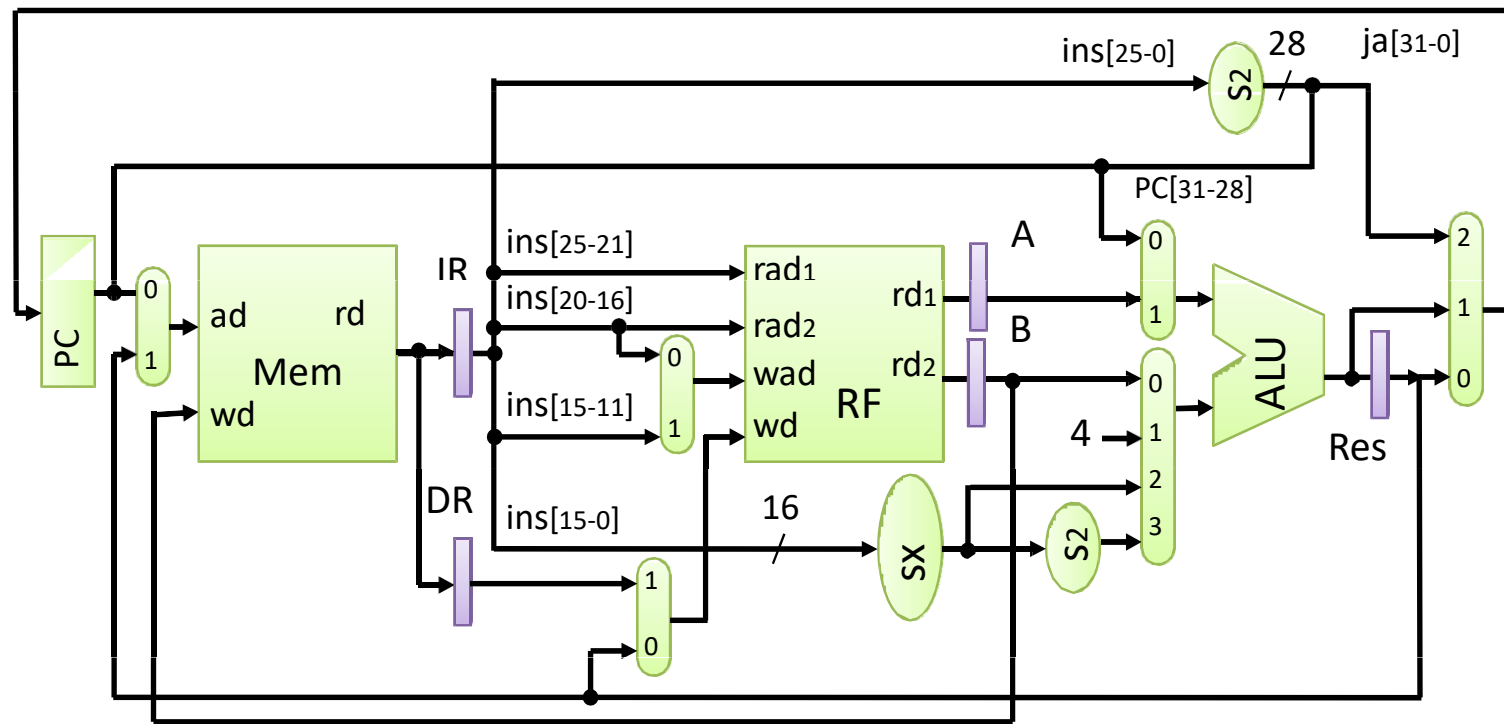
- Mux at Memory Input
- Mux at Register File Input
- One memory for lw / sw
- One ALU for EXE and Address Calculation
- Several MUXes introduced



MIPS Pipelined Datapath

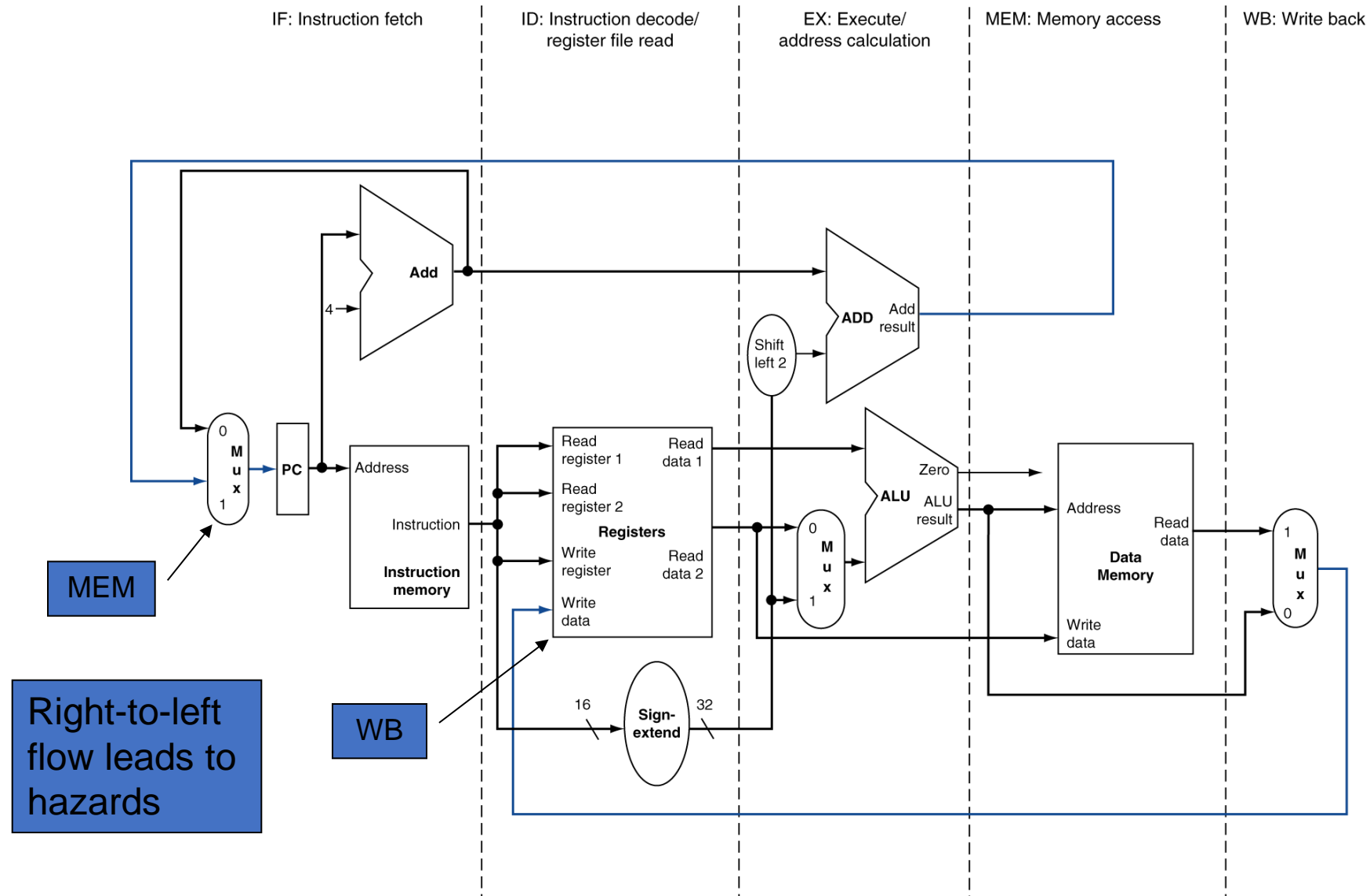

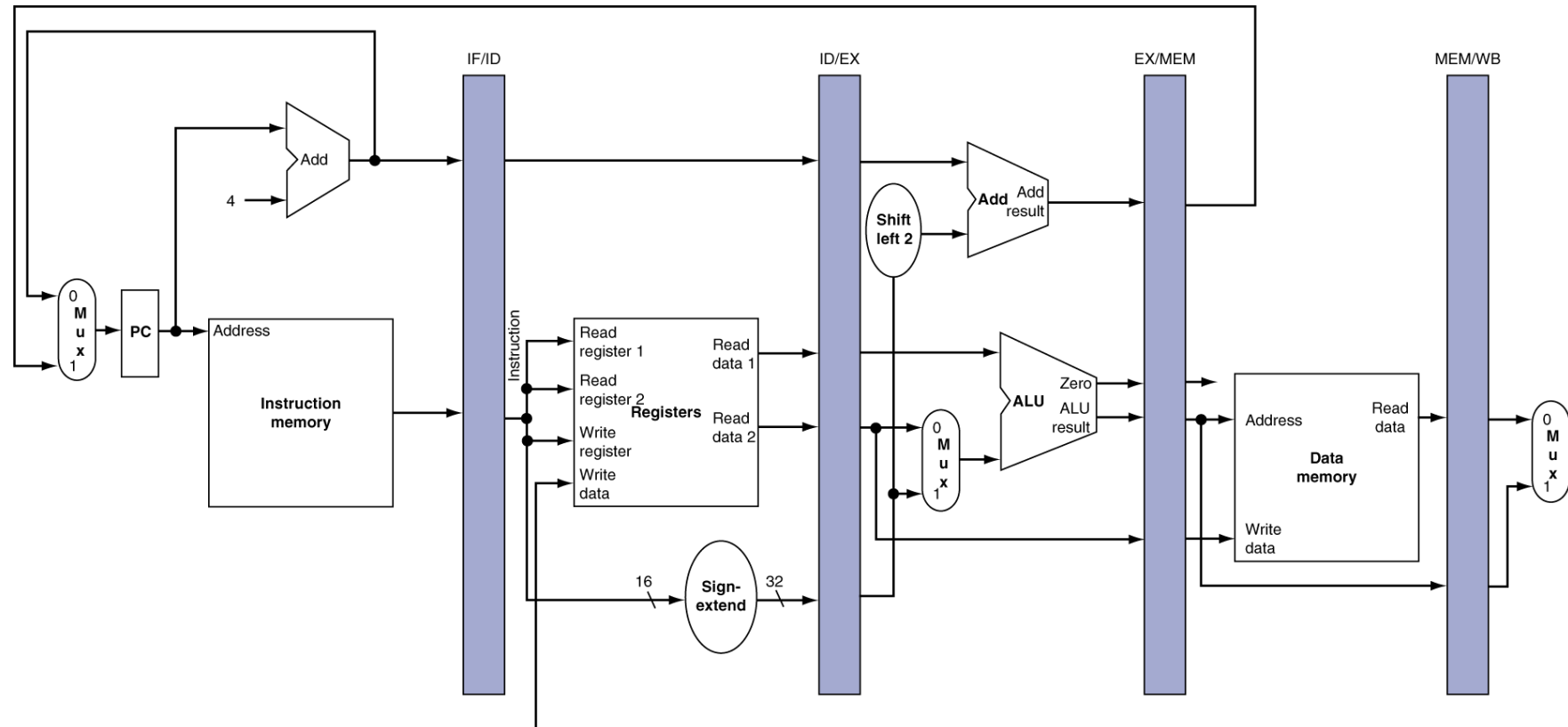- Need registers between stages
 - To hold information produced in previous cycle




- Cycle-by-cycle flow of instructions through the pipelined datapath
 - “Single-clock-cycle” pipeline diagram
 - Shows pipeline usage in a single cycle
 - Highlight resources used
 - c.f. “multi-clock-cycle” diagram
 - Graph of operation over time
- We’ll look at “single-clock-cycle” diagrams for load & store


RF is two operations in One Clock Cycle



 
- Assume Write is when clock is going up
 - Assume Read is when Clock is going down
- (you can assume otherwise too, but two operations in one clock cycle)




IF for Load, Store, ...

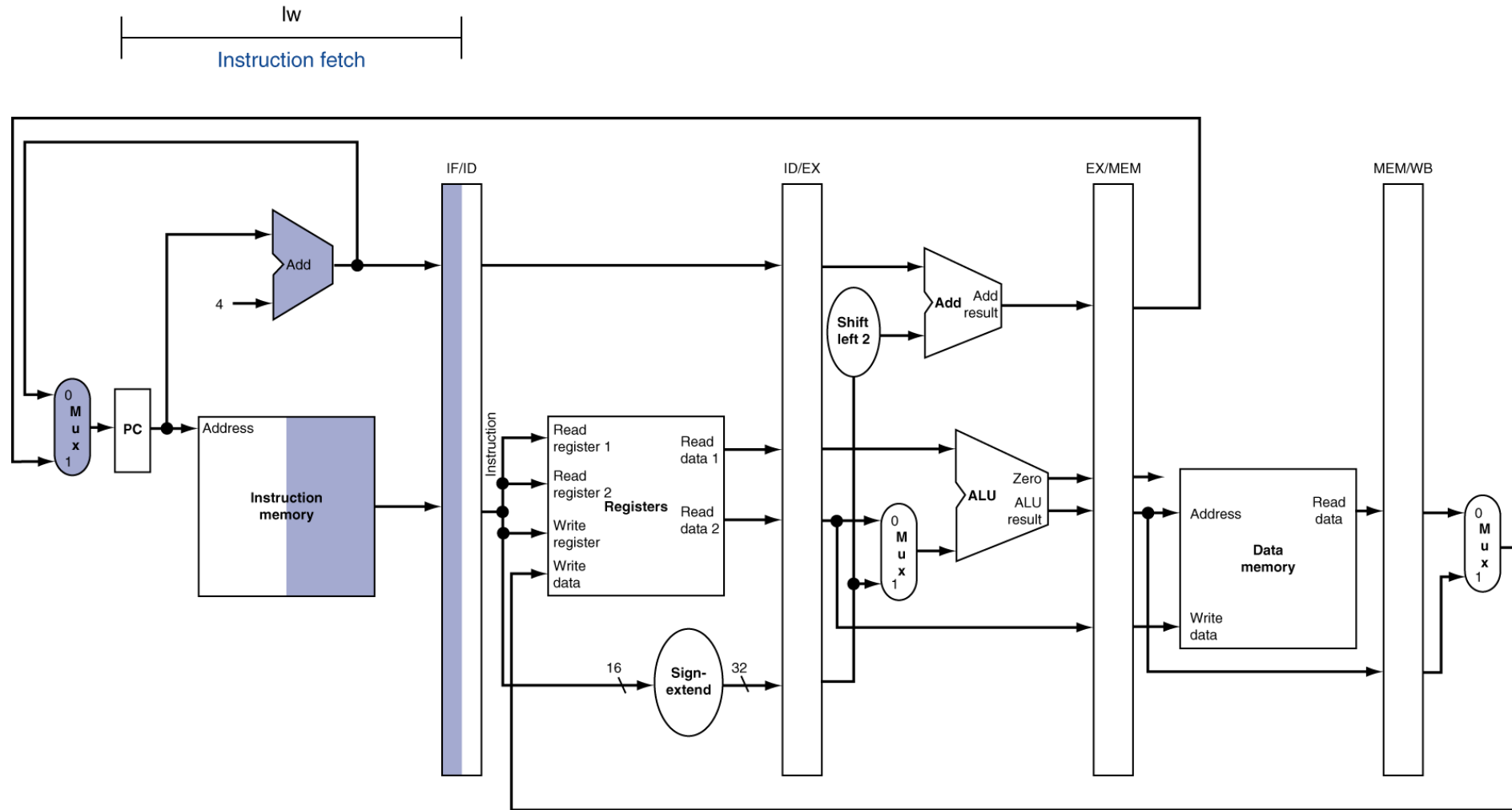


ID for Load, Store, ...

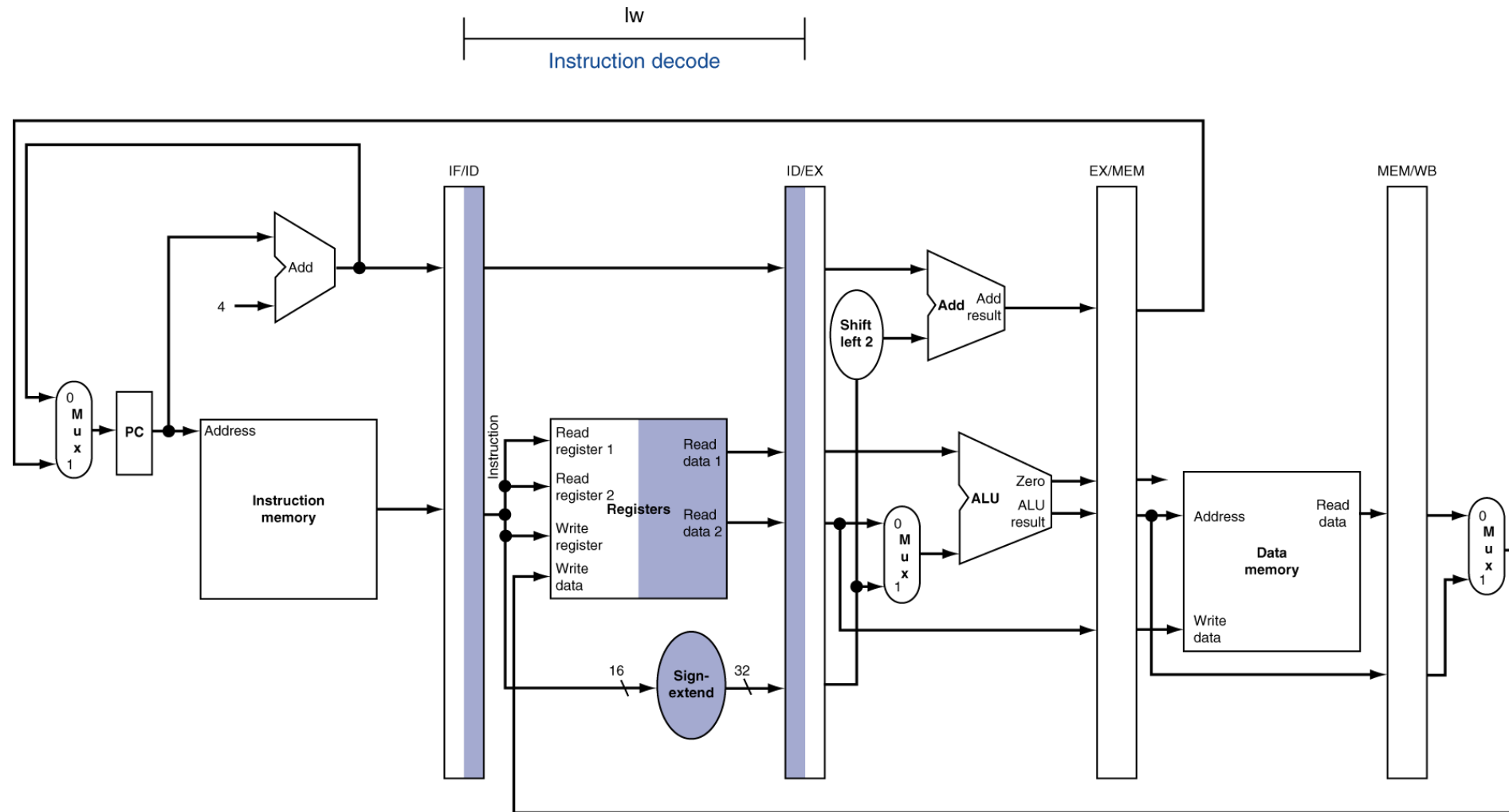


EX for Load

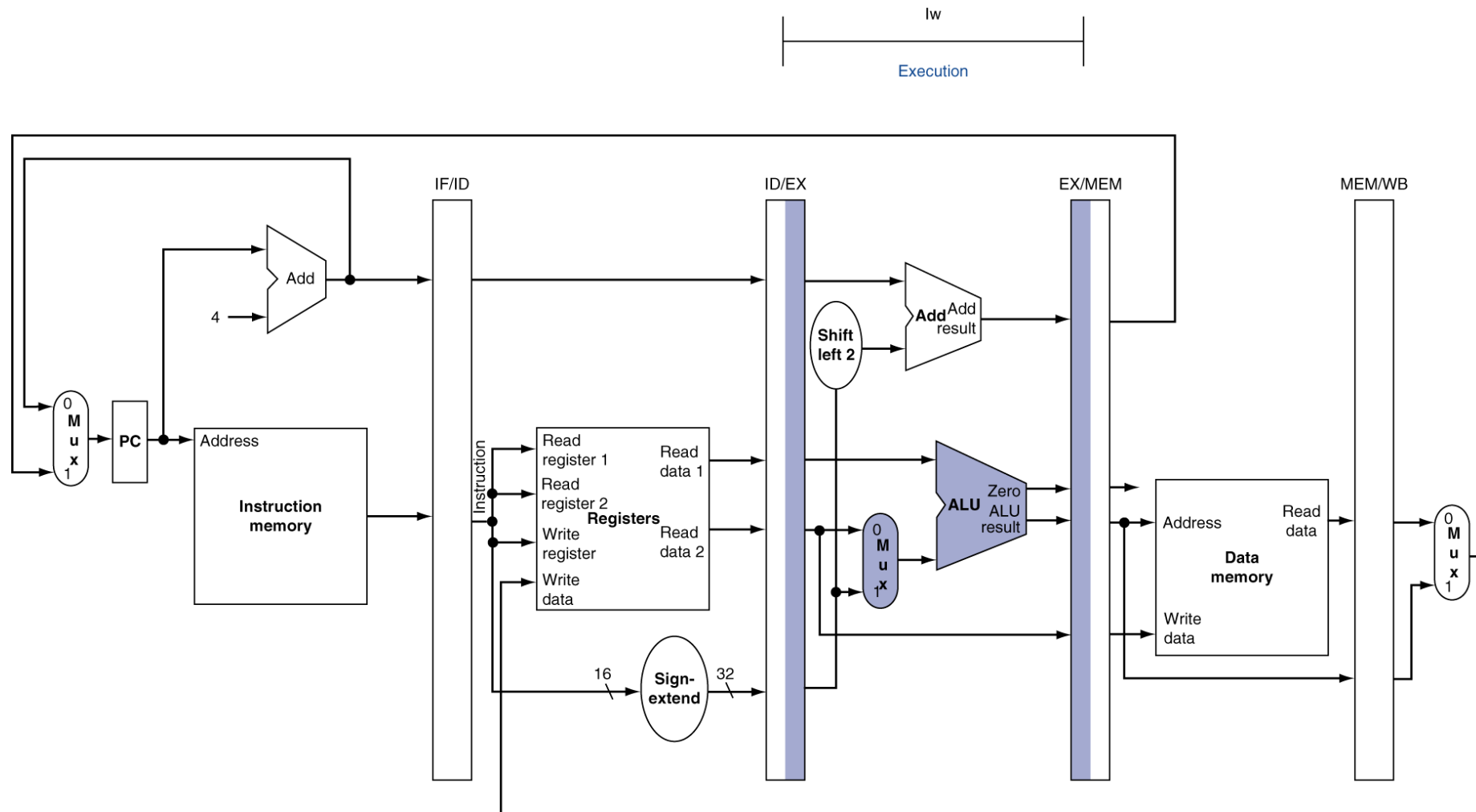


MEM for Load

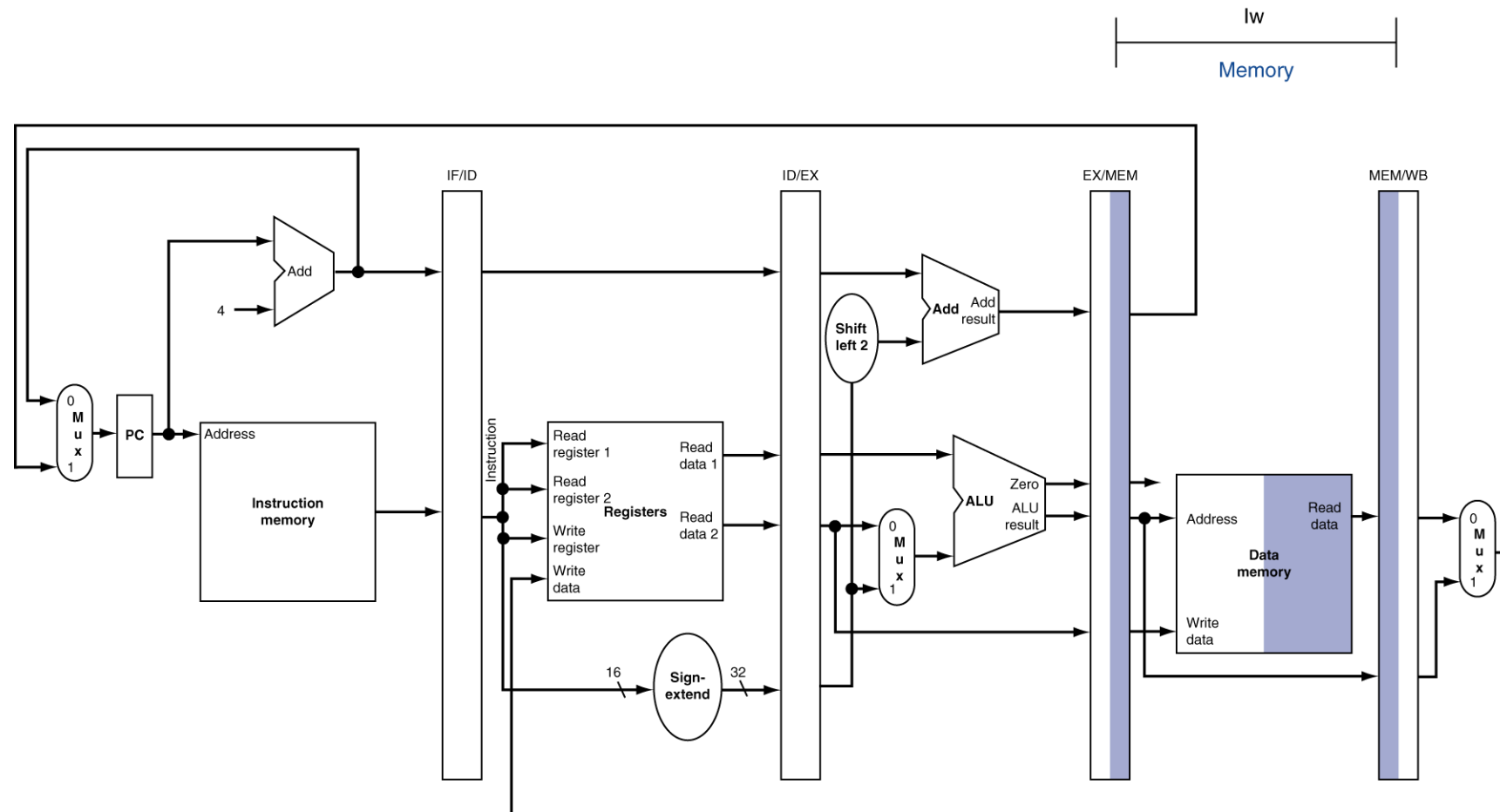


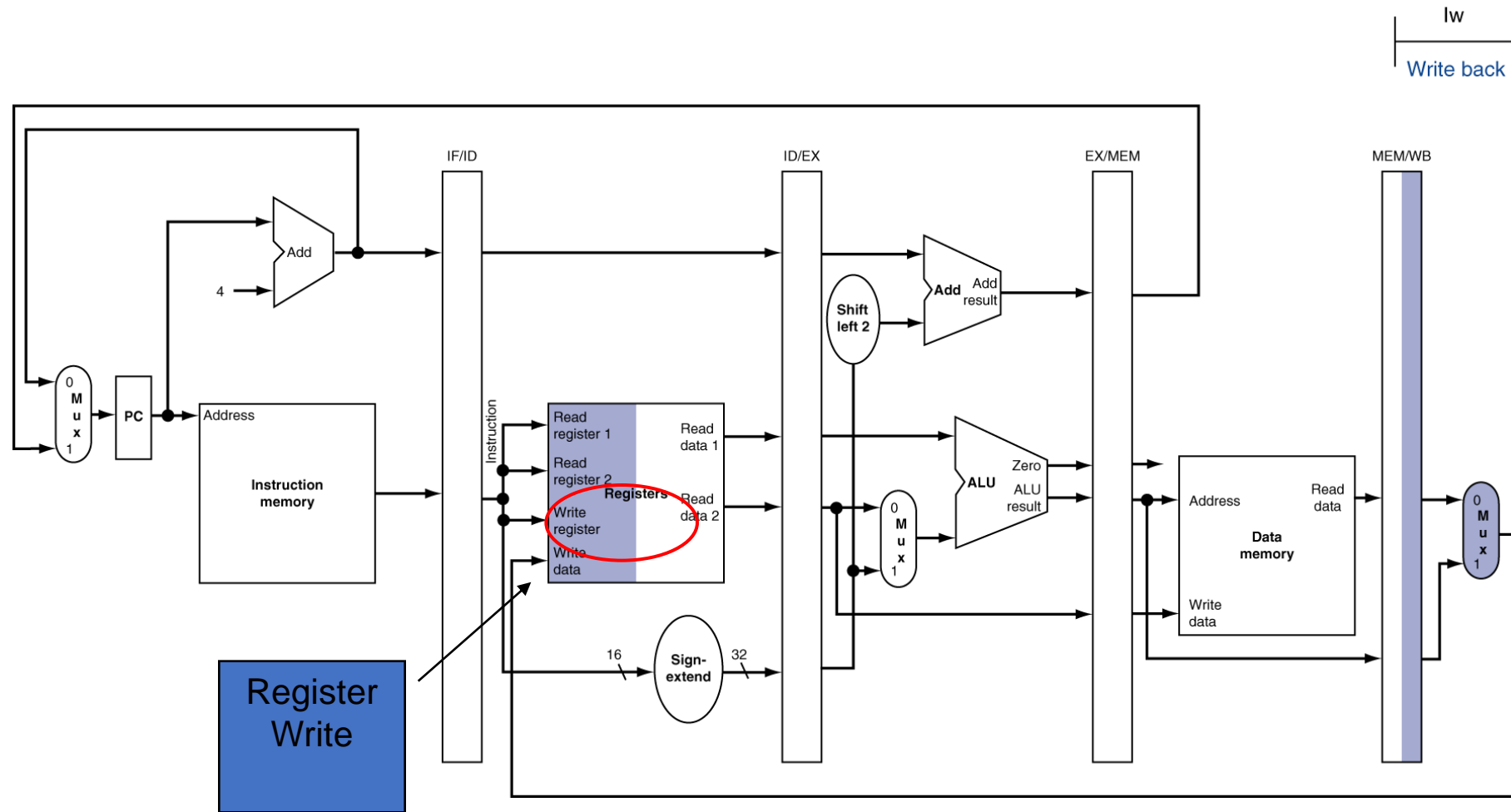


EX for Store

 


MEM for Store

 


 


Pipeline Registers

 

Pipelined MIPS Datapath

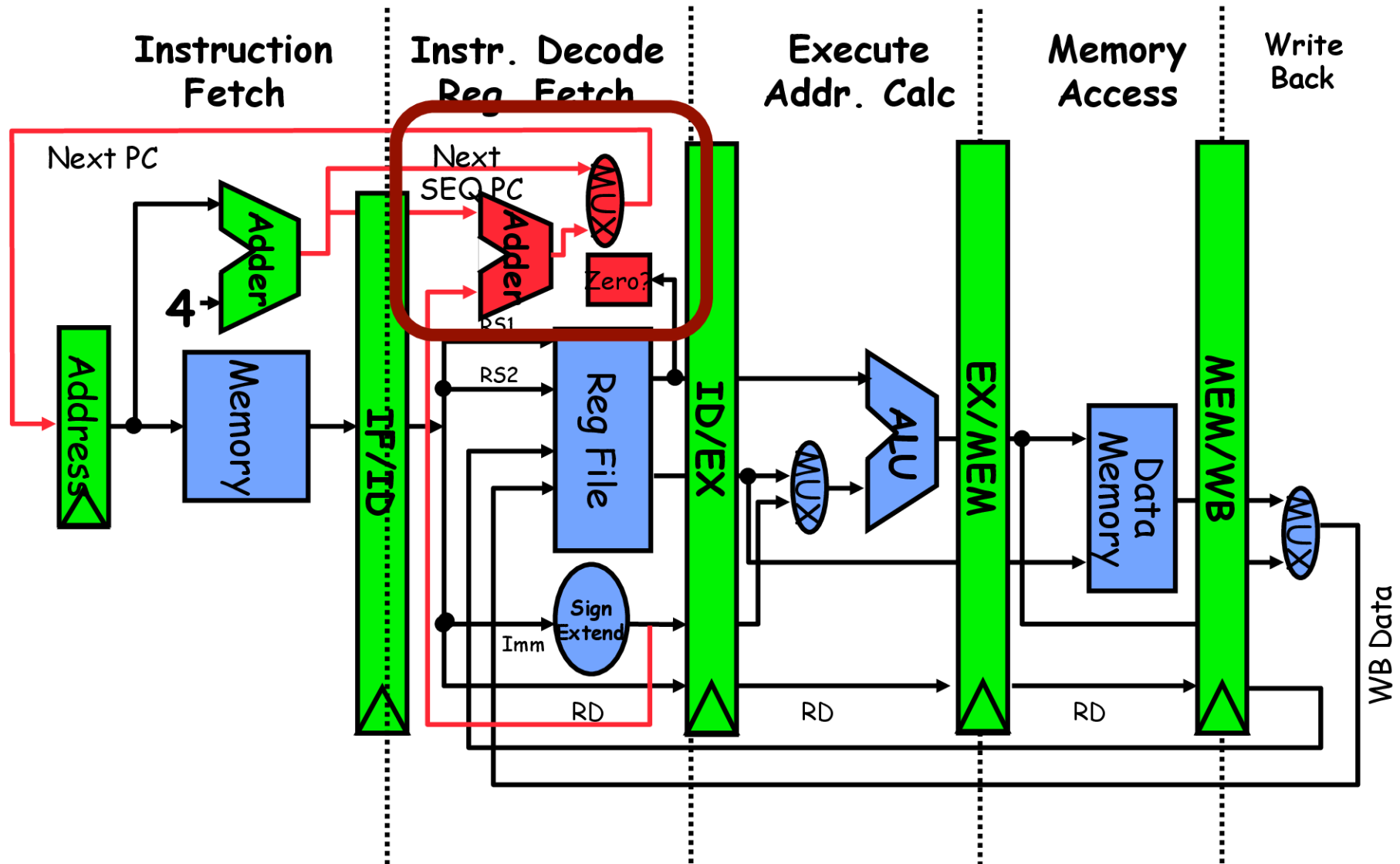

 
The Basic Pipeline For MIPS – Simplified Diagram



Multi-Cycle Pipeline Diagram




- Traditional form

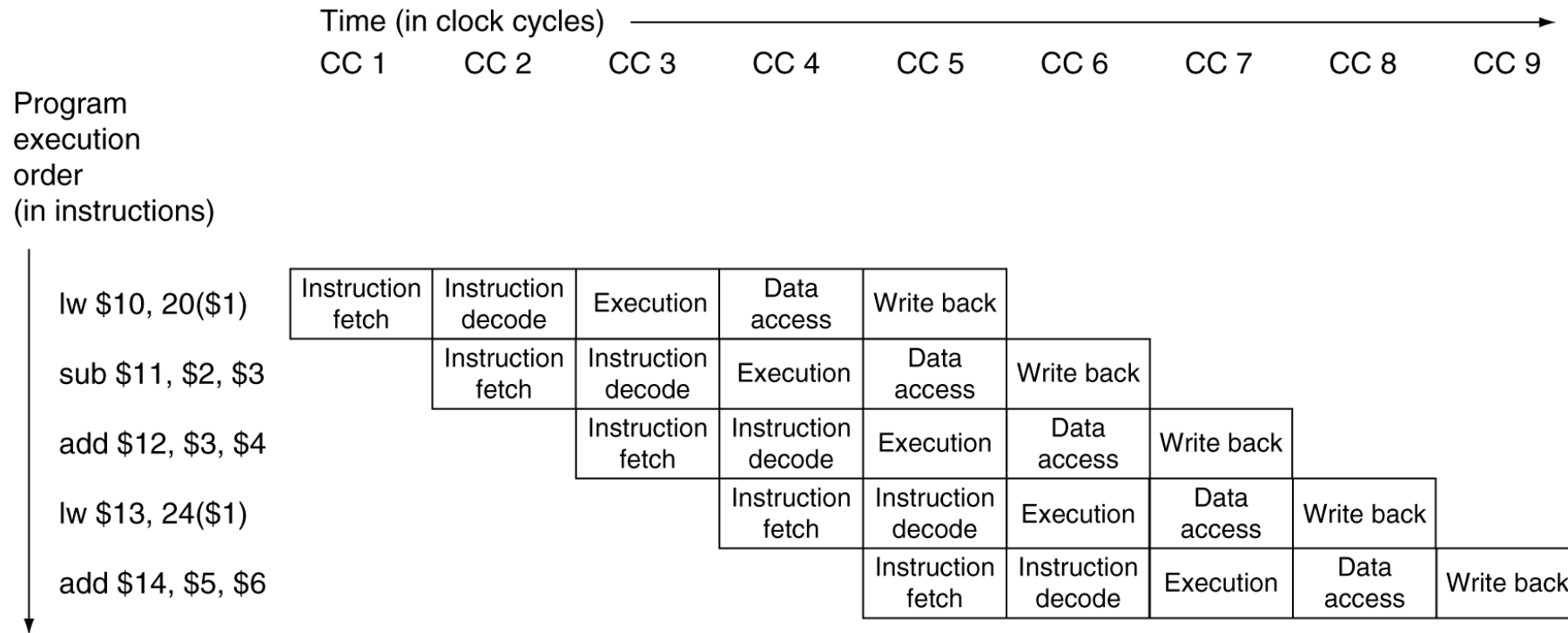

Multi-Cycle Pipeline Diagram

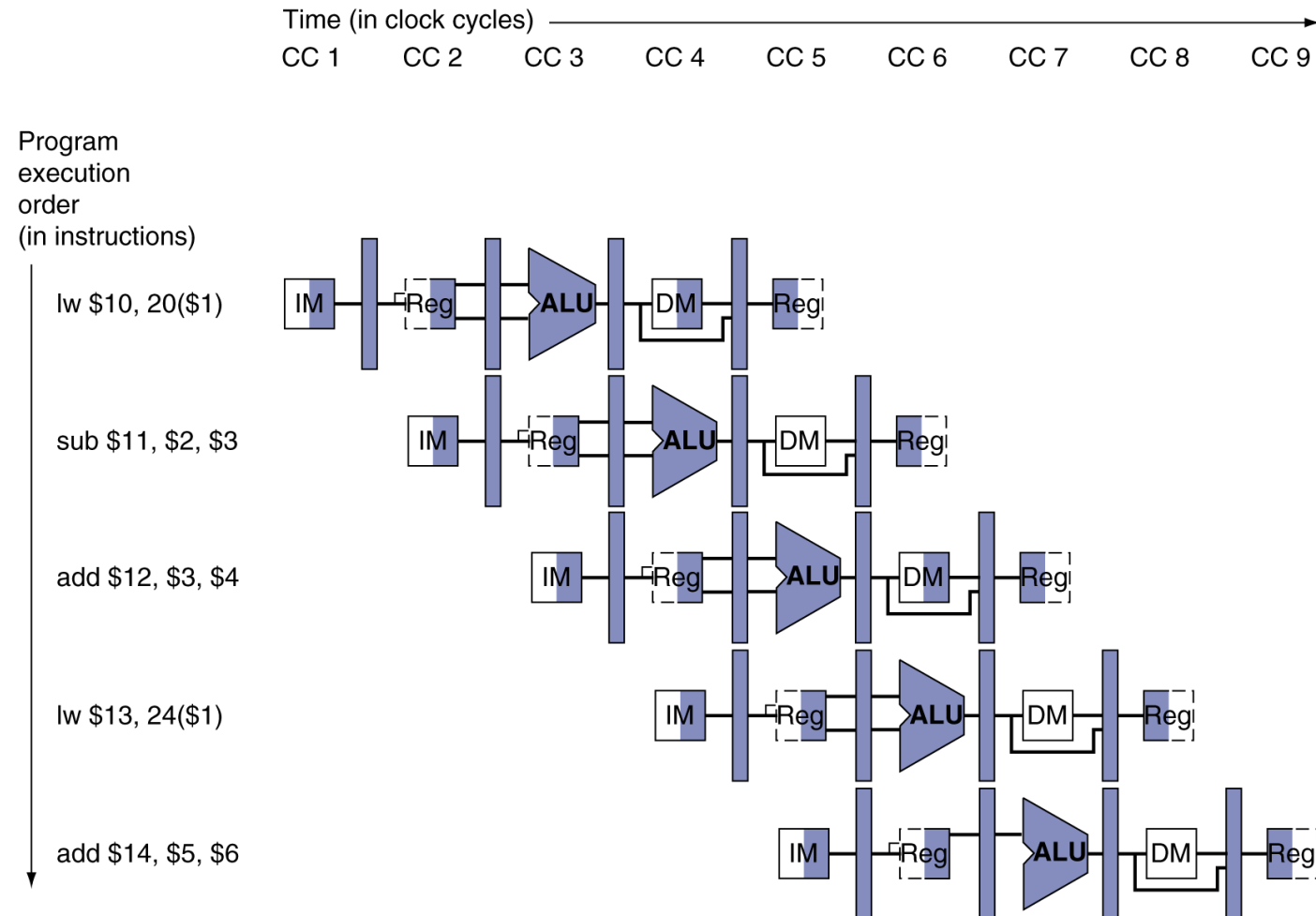
- Form showing resource usage for different instructions



Single-Cycle Pipelined Diagram



- State of pipeline in a given cycle

add \$14, \$5, \$6	lw \$13, 24 (\$1)	add \$12, \$3, \$4	sub \$11, \$2, \$3	lw \$10, 20(\$1)
Instruction fetch	Instruction decode	Execution	Memory	Write-back

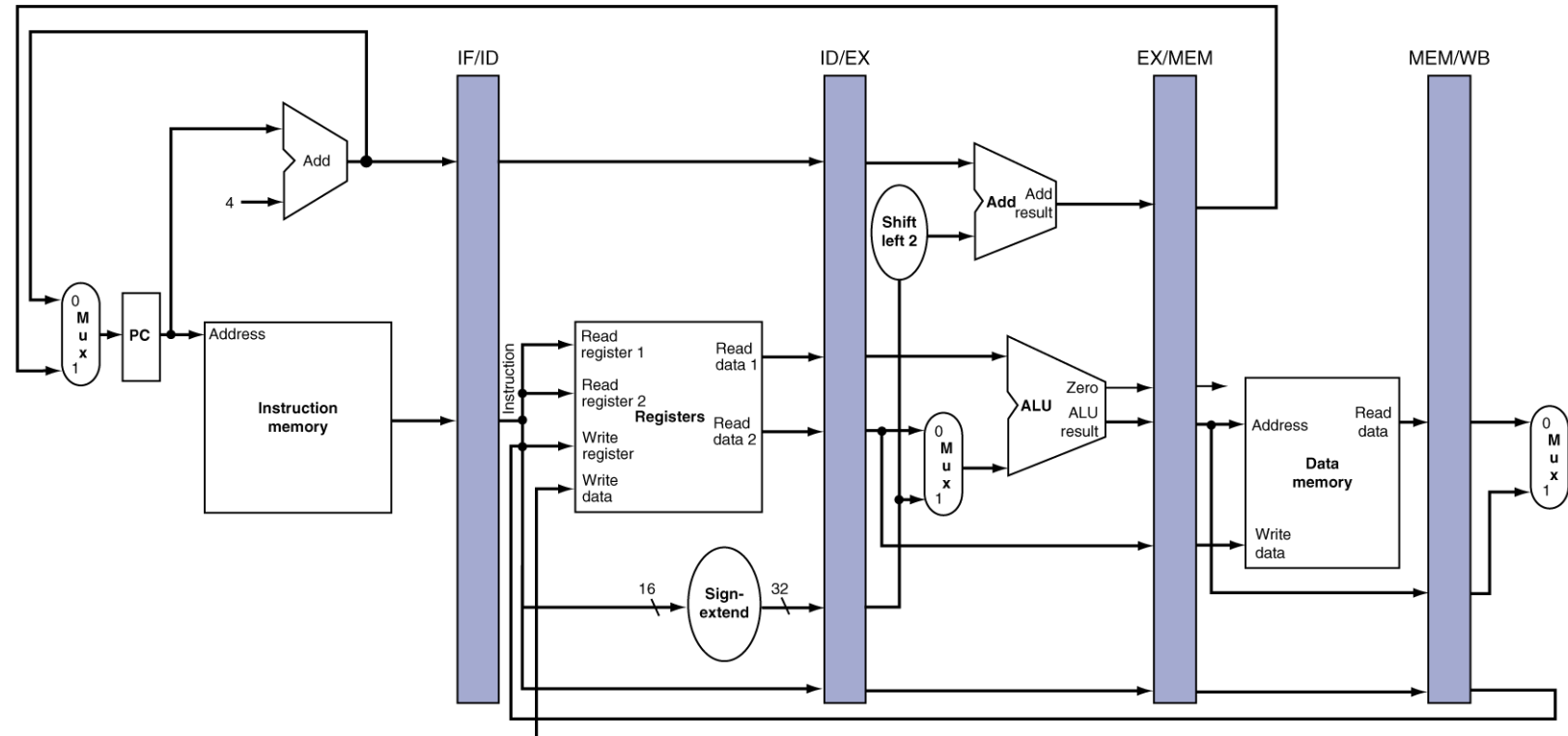

Pipeline Performance Estimation

  
- Pipelined laundry: overlapping execution
 - Parallelism improves performance



- Four loads:
 - Speedup
 $= 8 / 3.5 = 2.3$

D Example program


 
CT=1.5ns; CPU Time = $9 \times 1 \times 1.5\text{ns} = 13.5\text{ns}$



- Assume time for stages is
 - 100ps for register read or write
 - 200ps for other stages
- Compare pipelined datapath with single-cycle datapath

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps


Pipeline Performance

  


Multi-cycle Control Path

- Break instructions into cycles
- Put cycle sequences together
- Control signal groups and micro operations
- Control states and signal values
- Control state transitions

 - Control signals derived from instruction
 - As in single-cycle implementation



Pipelined Control with Connections

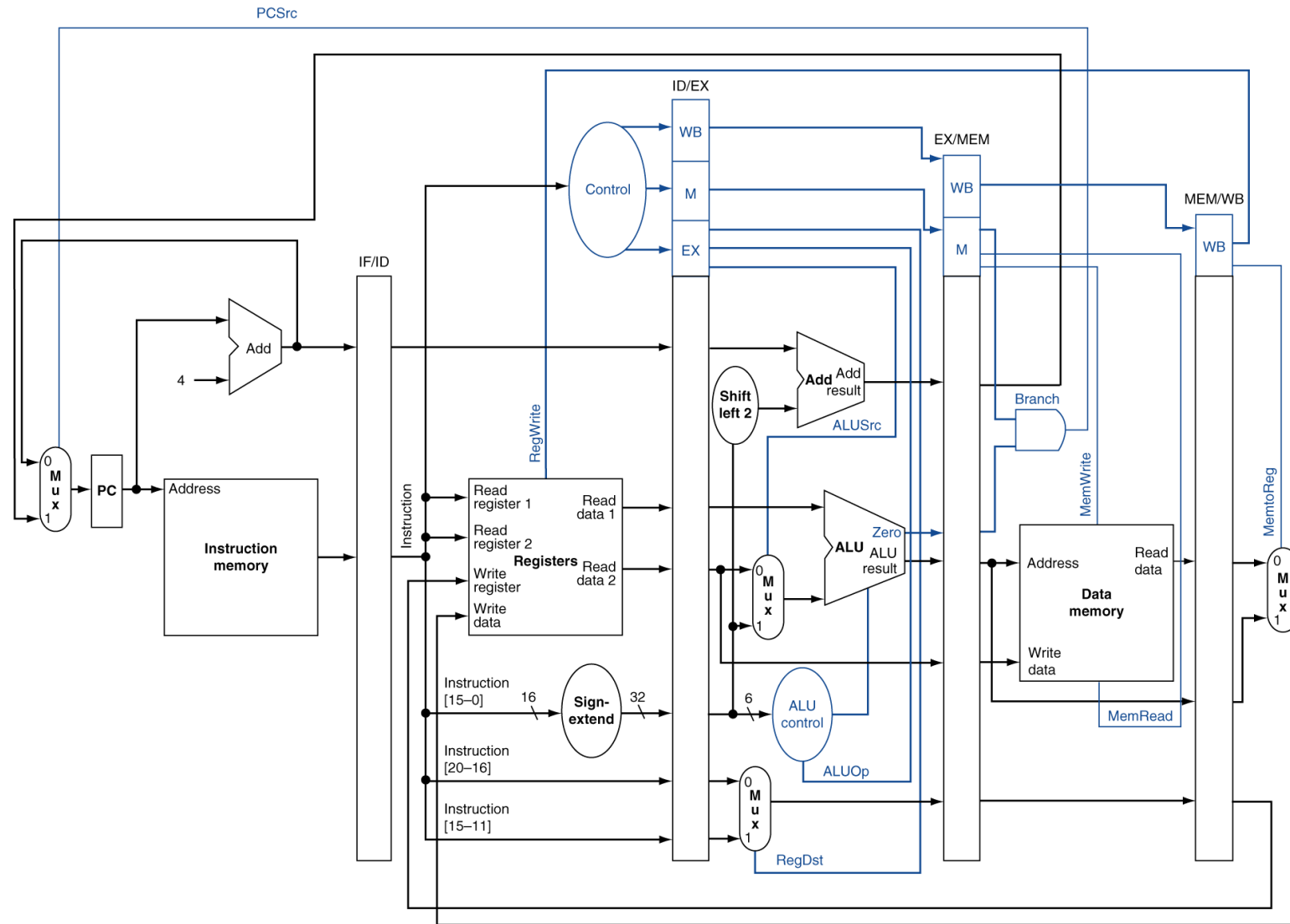

- Chap 4 of P&H Textbook