

# CS/EE 320 Computer Organization and Assembly Language Spring 2024

Shahid Masud

Lecture 9

- Logic and Arithmetic Instructions in Assembly Language
- Binary Numbers, Logic Design and Boolean Algebra
- Basic digital logic functions Invert, AND, OR, NAND, NOR
- Half-Adder (without Carry-In)
- 1-bit Full Adder (with Carry-In)
- Making 2's Complement Subtractor from Full-Adder
- Design of 1-bit ALU containing AND gate, OR gate, Full Adder
- Quiz 2 next lecture

# MIPS Arithmetic Instructions



Category	Instruction	Example	Meaning	Comments
Arithmetic	add	add \$s1,\$s2,\$s3	$\$s1 = \$s2 + \$s3$	Three operands; overflow detected
	subtract	sub \$s1,\$s2,\$s3	$\$s1 = \$s2 - \$s3$	Three operands; overflow detected
	add immediate	addi \$s1,\$s2,100	$\$s1 = \$s2 + 100$	+ constant; overflow detected
	add unsigned	addu \$s1,\$s2,\$s3	$\$s1 = \$s2 + \$s3$	Three operands; overflow undetected
	subtract unsigned	subu \$s1,\$s2,\$s3	$\$s1 = \$s2 - \$s3$	Three operands; overflow undetected
	add immediate unsigned	addiu \$s1,\$s2,100	$\$s1 = \$s2 + 100$	+ constant; overflow undetected
	move from coprocessor register	mfc0 \$s1,\$epc	$\$s1 = \$epc$	Copy Exception PC + special regs
	multiply	mult \$s2,\$s3	Hi, Lo = $\$s2 \times \$s3$	64-bit signed product in Hi, Lo
	multiply unsigned	multu \$s2,\$s3	Hi, Lo = $\$s2 \times \$s3$	64-bit unsigned product in Hi, Lo
	divide	div \$s2,\$s3	Lo = $\$s2 / \$s3$ , Hi = $\$s2 \bmod \$s3$	Lo = quotient, Hi = remainder
	divide unsigned	divu \$s2,\$s3	Lo = $\$s2 / \$s3$ , Hi = $\$s2 \bmod \$s3$	Unsigned quotient and remainder
	move from Hi	mfhi \$s1	$\$s1 = \text{Hi}$	Used to get copy of Hi
	move from Lo	mflo \$s1	$\$s1 = \text{Lo}$	Used to get copy of Lo

# MIPS Logical Instructions



Logical	AND	AND	$\$s1, \$s2, \$s3$	$\$s1 = \$s2 \& \$s3$	Three reg. operands; bit-by-bit AND
	OR	OR	$\$s1, \$s2, \$s3$	$\$s1 = \$s2 \mid \$s3$	Three reg. operands; bit-by-bit OR
	NOR	NOR	$\$s1, \$s2, \$s3$	$\$s1 = \sim (\$s2 \mid \$s3)$	Three reg. operands; bit-by-bit NOR
	AND immediate	ANDi	$\$s1, \$s2, 100$	$\$s1 = \$s2 \& 100$	Bit-by-bit AND with constant
	OR immediate	ORi	$\$s1, \$s2, 100$	$\$s1 = \$s2 \mid 100$	Bit-by-bit OR with constant
	shift left logical	sll	$\$s1, \$s2, 10$	$\$s1 = \$s2 \ll 10$	Shift left by constant
	shift right logical	srl	$\$s1, \$s2, 10$	$\$s1 = \$s2 \gg 10$	Shift right by constant


- Operations on integers
  - Addition and subtraction
  - Multiplication and division
  - Dealing with overflow
- Floating-point real numbers (later)
  - Representation and operations

# Basic Logic Operations in CPU




- Functions Through Logic Gates
  - NOT
  - AND
  - OR
  - NOR
  - NAND
  - XOR

# Gates (Primary Gates)

 


# Gates (Compound Gates)

 

AND Gate followed by Inverter

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 


OR Gate followed by Inverter

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0




Two Input Exclusive OR Gate

 


$$F = \bar{A}B + A\bar{B}$$

$$F = A \oplus B$$


A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

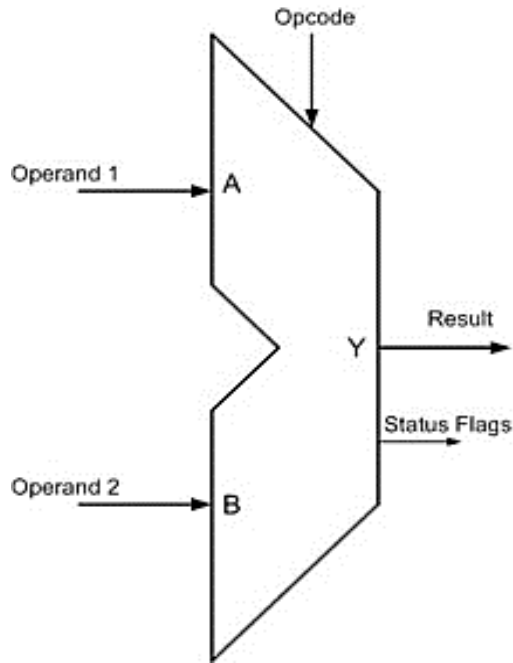

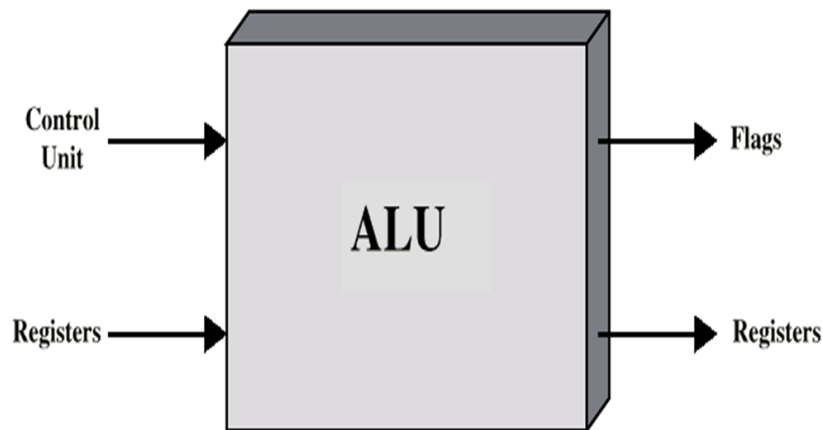- Does all calculations
- Everything else in the computer is there to service this unit
- Handles integers
- May handle floating point (real) numbers
- May be separate FPU (maths co-processor)
- May be on chip separate FPU (Eg. 486DX)



# ALU in **Load/Store** Architecture

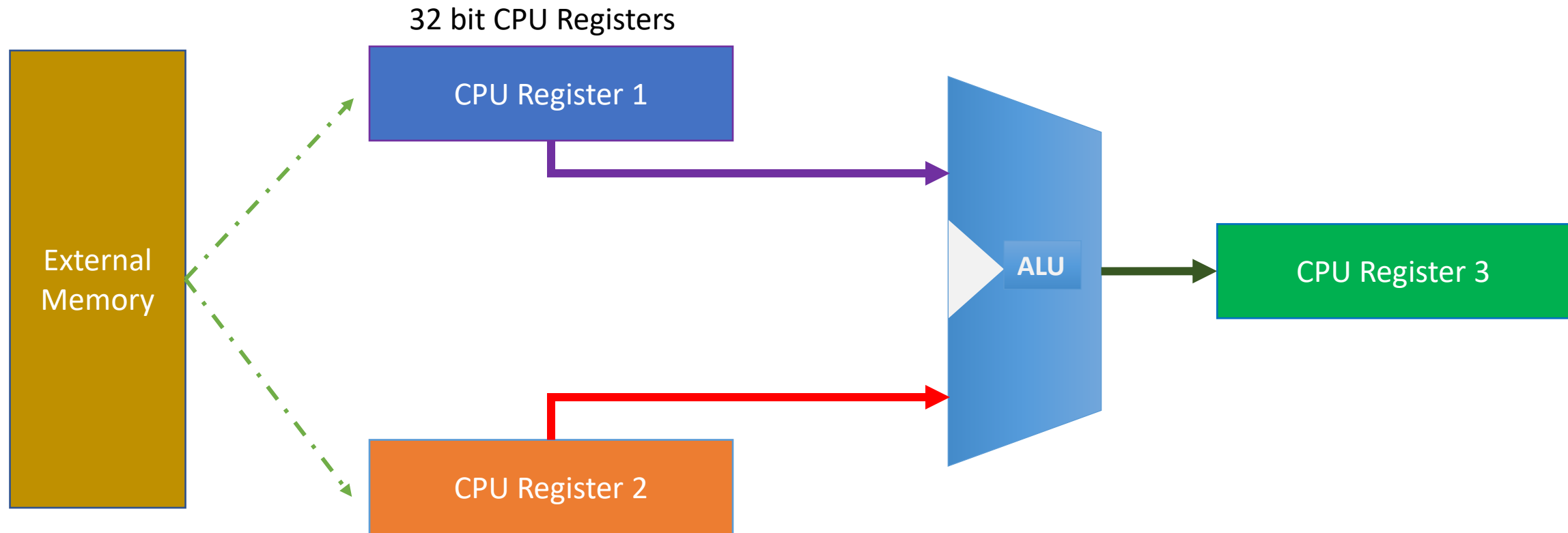

- ALU does calculations with binary numbers
- Decimal number system
  - Uses 10 digits (0,1,2,3,4,5,6,7,8,9)
  - In decimal system, a number 84, e.g., means
$$84 = (8 \times 10) + 4$$
  - $4728 = (4 \times 1000) + (7 \times 100) + (2 \times 10) + 8$
  - Base or radix of 10  $\rightarrow$  each digit in the number is multiplied by 10 raised to a power corresponding to that digit's position
  - E.g.  $83 = (8 \times 10^1) + (3 \times 10^0)$
  - $4728 = (4 \times 10^3) + (7 \times 10^2) + (2 \times 10^1) + (8 \times 10^0)$

- Uses only two digits, 0 and 1
- It is base or radix of 2
- Each digit has a **value** depending on its **position**:
  - $10_2 = (1 \times 2^1) + (0 \times 2^0) = 2_{10}$
  - $11_2 = (1 \times 2^1) + (1 \times 2^0) = 3_{10}$
  - $100_2 = (1 \times 2^2) + (0 \times 2^1) + (0 \times 2^0) = 4_{10}$
  - $1001.101_2 = (1 \times 2^3) + (0 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) + (1 \times 2^{-1}) + (0 \times 2^{-2}) + (1 \times 2^{-3}) = 9.625_{10}$


# Decimal to Binary conversion



- Integer and fractional parts are handled separately,
  - Integer part is handled by repeating division by 2
  - Fractional part is handled by repeating multiplication by 2
- E.g. convert decimal 11.81 to binary
  - Integer part 11
  - Fractional part .81

- Fractional values, e.g.

 - $472.83 = (4 \times 10^2) + (7 \times 10^1) + (2 \times 10^0) + (8 \times 10^{-1}) + (3 \times 10^{-2})$



- In general, for the decimal representation of
- $X = \{ \dots x_2 x_1 x_0 . x_{-1} x_{-2} x_{-3} \dots \}$

$$X = \sum_i x_i 10^i$$

# Decimal to Binary conversion example



- e.g. 11.81 to 1011.11001 (approx)
  - $11/2 = 5$  remainder 1
  - $5/2 = 2$  remainder 1
  - $2/2 = 1$  remainder 0
  - $1/2 = 0$  remainder 1
  - Binary number 1011
  - $.81 \times 2 = 1.62$  integral part 1
  - $.62 \times 2 = 1.24$  integral part 1
  - $.24 \times 2 = 0.48$  integral part 0
  - $.48 \times 2 = 0.96$  integral part 0
  - $.96 \times 2 = 1.92$  integral part 1
  - Binary number .11001 (approximate)



- Compact representation of bus information
- Use 16 digits, (0,1,3,...9,A,B,C,D,E,F)
- $1A_{16} = (1_{16} \times 16^1) + (A_{16} \times 16^0)$   
 $= (1_{10} \times 16^1) + (10_{10} \times 16^0) = 26_{10}$
- Convert group of four binary digits to/from one hexadecimal digit,
  - 0000=0; 0001=1; 0010=2; 0011=3; 0100=4; 0101=5; 0110=6; 0111=7; 1000=8; 1001=9; 1010=A; 1011=B; 1100=C; 1101=D; 1110=E; 1111=F;
- e.g.
  - 1101 1110 0001. 1110 1101 = DE1.DE

- Only have 0 & 1 to represent everything
- Positive numbers stored in binary
  - e.g. 41=00101001
- No minus sign
- No period
- **How to represent negative number?**
  - Sign-Magnitude
  - Two's compliment

# Sign-Magnitude Representation



- Add one extra bit on MSB to represent sign
- Left most bit is sign bit
- 0 means positive
- 1 means negative
- $+18 = 00010010$
- $-18 = 10010010$
- Problems
  - Need to consider both sign and magnitude in arithmetic
  - Two representations of zero (+0 and -0)

# Two's Complement Representation



- $+3 = 00000011$
- $+2 = 00000010$
- $+1 = 00000001$
- $+0 = 00000000$
- $-1 = 11111111$
- $-2 = 11111110$
- $-3 = 11111101$

# 2's Complement Number System



- One representation of zero
- Arithmetic works easily, use same hardware as positive numbers
- Negating is fairly easy (2's complement operation)
  - 3 = 00000011
  - Boolean **complement** gives 11111100
  - Add +1 to LSB 11111101

# Range of 2's Complement Numbers



- 8 bit 2's complement
  - $+127 = 01111111 = 2^7 - 1$
  - $-128 = 10000000 = -2^7$
- 16 bit 2's complement
  - $+32767 = 01111111 11111111 = 2^{15} - 1$
  - $-32768 = 10000000 00000000 = -2^{15}$

# Different word lengths in 2's Complement



- Positive number pack with leading zeros
- $+18 =$              $00010010$  (in 8 bits)
- $+18 = 00000000\ 00010010$  (in 16 bits)
- Negative numbers pack with leading ones
- $-18 =$              $10010010$  (in 8 bits)
- $-18 = 11111111\ 10010010$  (in 16 bits, notice sign bit replication)
- i.e. pack higher bits with MSB (sign bit)

# Negation Special Case 1




- 0 = 00000000
- Bitwise not 11111111
- Add 1 to LSB +1
- Result 1 00000000
- **Overflow** is ignored, so:
- - 0 = 0 OK!



- $-128 = 10000000$
- bitwise not  $01111111$
- Add 1 to LSB  $+1$
- Result  $10000000$
- So:
- $-(-128) = -128$  **Problem here!**
- Monitor MSB (sign bit)
- It should change during negation
- >> There is no representation of  $+128$  in this case. (no  $+2^n$ )

- Normal binary addition
- $0011 \quad 0101 \quad 1100$
- $+0100 \quad +0100 \quad +1111$
- -----
- $0111 \quad \underline{1}001 = \text{overflow} \quad \underline{1}1011$
- Monitor sign bit for overflow (sign bit change as adding two positive numbers or two negative numbers.)
- Subtraction: Take twos complement of subtrahend then add to minuend
  - i.e.  $a - b = a + (-b)$
- **So we only need addition and complement circuits**

# Hardware for Addition and Subtraction

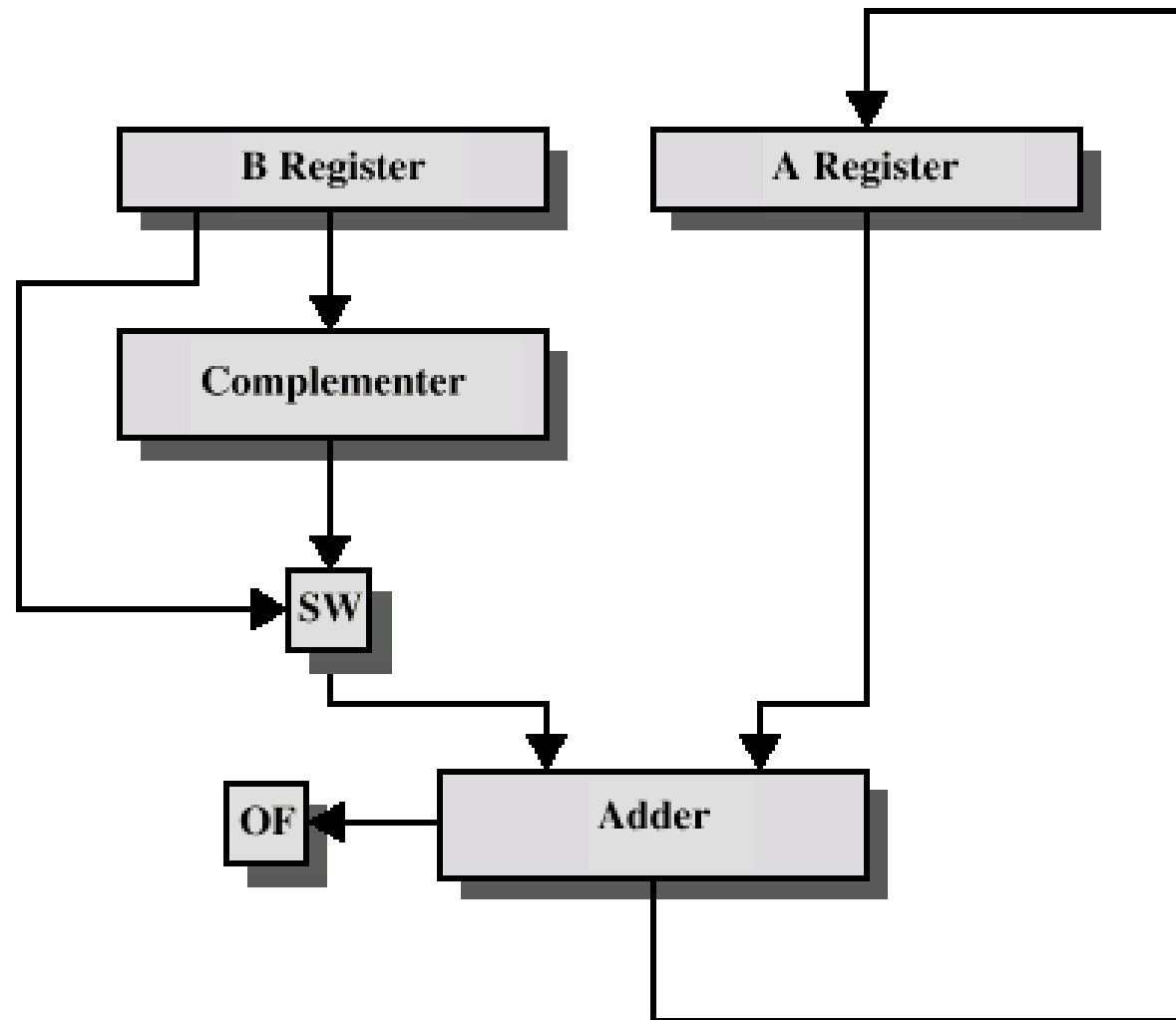


OF = overflow bit

SW = Switch (select addition or subtraction)

# Integer Addition - Overflow

- Example:  $7 + 6$

 

- **Overflow** if result is out of range
  - Adding +ve and -ve operands, no overflow
  - Adding two +ve operands
    - Overflow if result sign is 1
  - Adding two -ve operands
    - Overflow if result sign is 0

# Integer Subtraction - Overflow



- Add negation of second operand
- Example:  $7 - 6 = 7 + (-6)$ 
  - +7:      0000 0000 ... 0000 0111
  - -6:      1111 1111 ... 1111 1010
  - +1:      0000 0000 ... 0000 0001
- **Overflow** if result is out of range
  - Subtracting two +ve or two -ve operands, no overflow
  - Subtracting +ve from -ve operand
    - Overflow if result sign is 0
  - Subtracting -ve from +ve operand
    - Overflow if result sign is 1

# Overflow in Addition / Subtraction

**OVERFLOW RULE:** If two numbers are added, and they are both positive or both negative, then overflow occurs if and only if the result has the opposite sign.

$\begin{array}{r} 1001 = -7 \\ + 0101 = 5 \\ \hline 1110 = -2 \end{array}$ <p>(a) <math>(-7) + (+5)</math></p>	$\begin{array}{r} 1100 = -4 \\ + 0100 = 4 \\ \hline 10000 = 0 \end{array}$ <p>(b) <math>(-4) + (+4)</math></p>
$\begin{array}{r} 0011 = 3 \\ + 0100 = 4 \\ \hline 0111 = 7 \end{array}$ <p>(c) <math>(+3) + (+4)</math></p>	$\begin{array}{r} 1100 = -4 \\ + 1111 = -1 \\ \hline 11011 = -5 \end{array}$ <p>(d) <math>(-4) + (-1)</math></p>
$\begin{array}{r} 0101 = 5 \\ + 0100 = 4 \\ \hline 1001 = \text{Overflow} \end{array}$ <p>(e) <math>(+5) + (+4)</math></p>	$\begin{array}{r} 1001 = -7 \\ + 1010 = -6 \\ \hline 10011 = \text{Overflow} \end{array}$ <p>(f) <math>(-7) + (-6)</math></p>

**Figure 10.3** Addition of Numbers in Twos Complement Representation

$\begin{array}{r} 0010 = 2 \\ + 1001 = -7 \\ \hline 1011 = -5 \end{array}$ <p>(a) <math>M = 2 = 0010</math>  <math>S = 7 = 0111</math>  <math>-S = 1001</math></p>	$\begin{array}{r} 0101 = 5 \\ + 1110 = -2 \\ \hline 10011 = 3 \end{array}$ <p>(b) <math>M = 5 = 0101</math>  <math>S = 2 = 0010</math>  <math>-S = 1110</math></p>
$\begin{array}{r} 1011 = -5 \\ + 1110 = -2 \\ \hline 11001 = -7 \end{array}$ <p>(c) <math>M = -5 = 1011</math>  <math>S = 2 = 0010</math>  <math>-S = 1110</math></p>	$\begin{array}{r} 0101 = 5 \\ + 0010 = 2 \\ \hline 0111 = 7 \end{array}$ <p>(d) <math>M = 5 = 0101</math>  <math>S = -2 = 1110</math>  <math>-S = 0010</math></p>
$\begin{array}{r} 0111 = 7 \\ + 0111 = 7 \\ \hline 1110 = \text{Overflow} \end{array}$ <p>(e) <math>M = 7 = 0111</math>  <math>S = -7 = 1001</math>  <math>-S = 0111</math></p>	$\begin{array}{r} 1010 = -6 \\ + 1100 = -4 \\ \hline 10110 = \text{Overflow} \end{array}$ <p>(f) <math>M = -6 = 1010</math>  <math>S = 4 = 0100</math>  <math>-S = 1100</math></p>

**Figure 10.4** Subtraction of Numbers in Twos Complement Representation ( $M - S$ )

- Some languages (e.g., C) ignore overflow
  - Use MIPS addu, addui, subu instructions
- Other languages (e.g., Ada, Fortran) require raising an exception
  - Use MIPS add, addi, sub instructions
  - On overflow, invoke exception handler
    - Save PC in exception program counter (EPC) register
    - Jump to predefined handler address
    - mfc0 (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action

The computer designer must therefore provide a way to ignore overflow in some cases and to recognize it in others. The MIPS solution is to have two kinds of arithmetic instructions to recognize the two choices:

- Add (`add`), add immediate (`addi`), and subtract (`sub`) cause exceptions on overflow.
- Add unsigned (`addu`), add immediate unsigned (`addiu`), and subtract unsigned (`subu`) do *not* cause exceptions on overflow.


Because C ignores overflows, the MIPS C compilers will always generate the unsigned versions of the arithmetic instructions `addu`, `addiu`, and `subu`, no matter what the type of the variables. The MIPS Fortran compilers, however, pick the appropriate arithmetic instructions, depending on the type of the operands.



# Logic Circuit of Adder / Subtractor
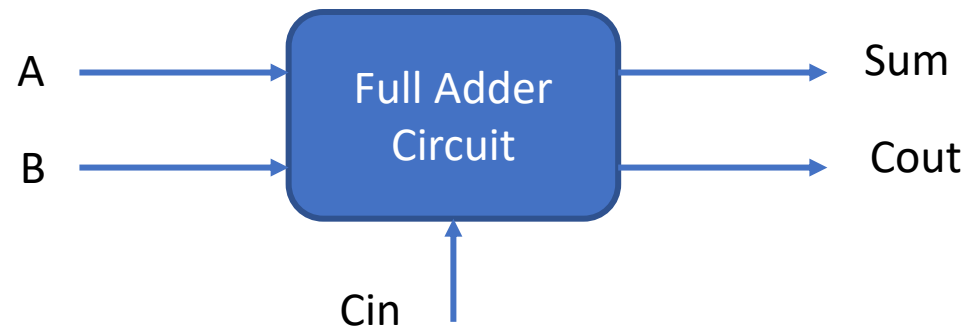
# 1 Bit Full Adder Circuit

Truth table represents **behaviour** of inputs and outputs




A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Expression:


$$\text{Sum } S_i = X_i \oplus Y_i \oplus C_i$$

$$C_{i+1} = X_i \cdot Y_i + C_i (X_i \oplus Y_i)$$
 
# Full Adder Implementation using Logic Gates



$$Sum = A \oplus B \oplus Cin$$

 


$$Cout = AB + ACin + BCin$$

 
# Array of Adders?

Usually, data types defined in any program are 8 bits, 16 bits or 32 bits


We need array of arithmetic and logic circuits to perform ALU operation on CPU registers



# Multiple Bits – Ripple Carry Adder

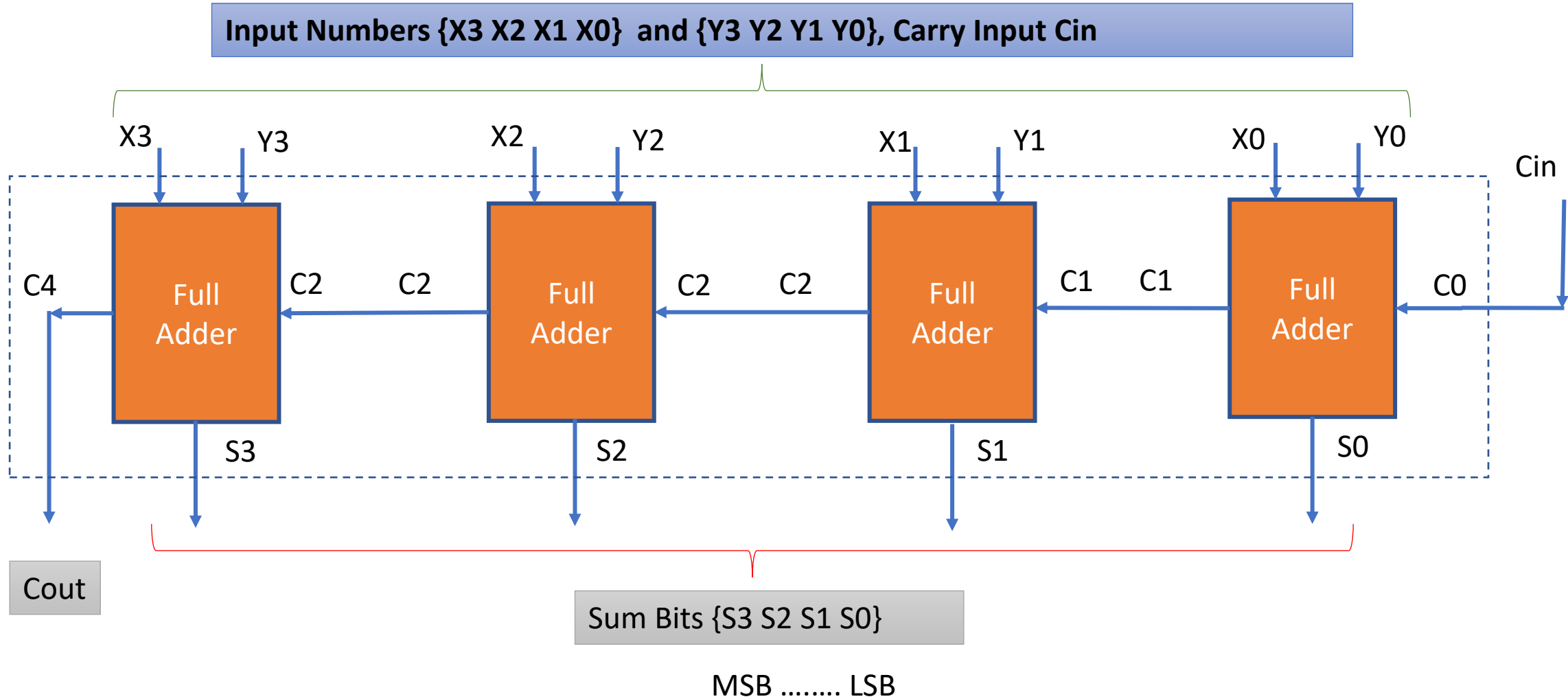
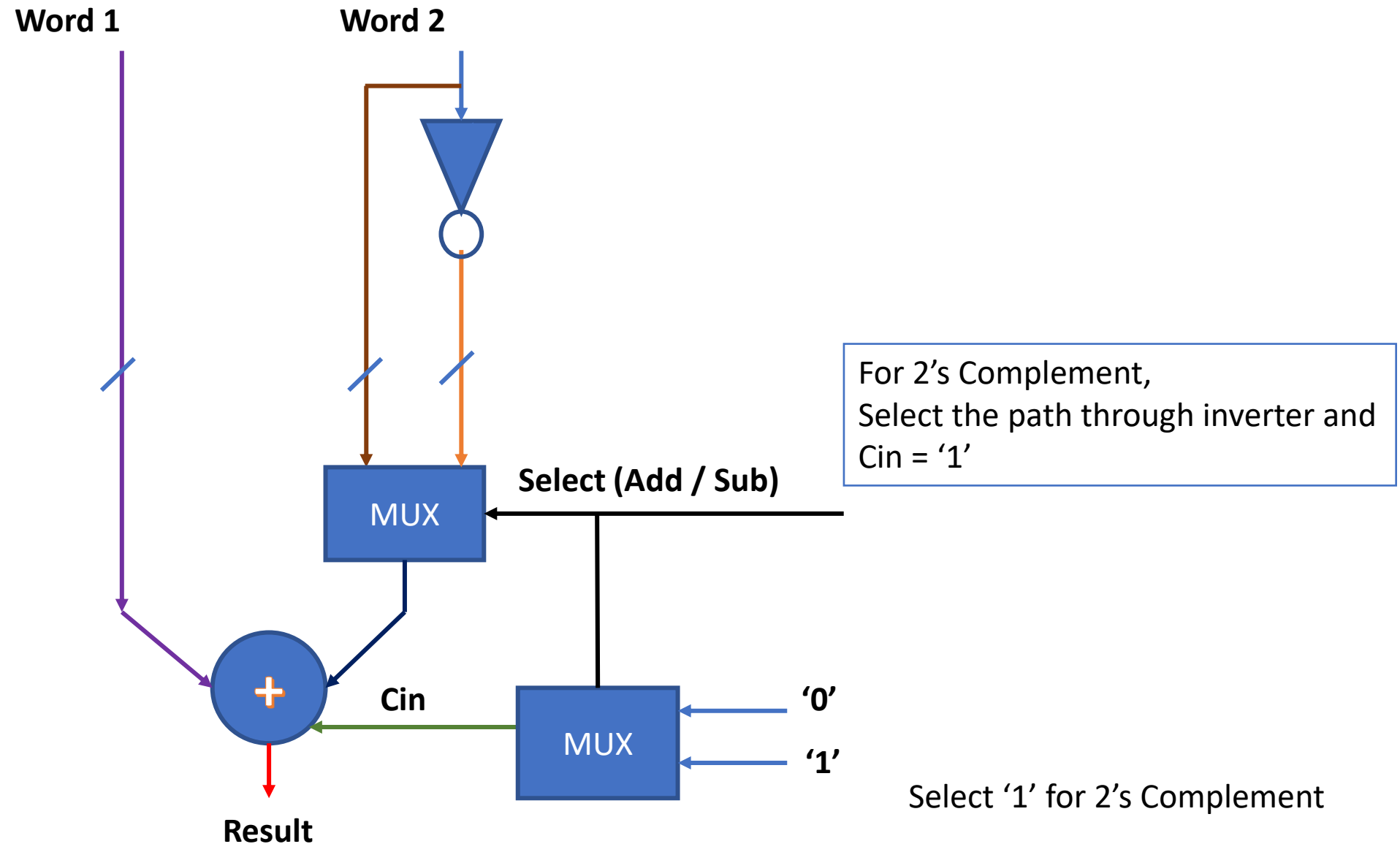
# Combined Adder and 2's Complement Subtraction



- P&H Textbook Chapter 3
- Search Appendix C P&H Textbook online; this contains useful background material on digital logic, ALU and related stuff