

CS / EE 320 Computer Organization and Assembly Language Spring 2025

Shahid Masud

Topics: Introduction to Full CPU Design – Simple 1 Bit ALU, Scaling to 32 Bit ALU

Topics



- Start Chapter 4 of P&H Textbook
- Some material in Appendix B of P&H Textbook, search Internet
- Digital Elements that Preserve States (D Flip Flops)
- CPU visualization as Combinational Element placed between two state elements, the Data path and Control path
- Develop a 1 Bit ALU and scale up to 32 Bits
- Basic Operations of ALU, AND, OR, ADD, SUB, NAND, NOR, Zero Detect, Compare, Overflow Detect
- QUIZ 3 NEXT LECTURE

Simple Processor Design




- MIPS subset for implementation
- Design overview
- Division into data path and control
- Building blocks combinational and sequential
- Clock and timings
- Components required for MIPS subset


Combinational Elements




- AND-gate
 - Y = A & B

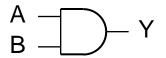

- Multiplexer
 - Y = S ? I1 : I0

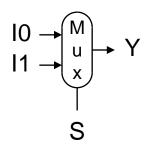


•
$$Y = A + B$$

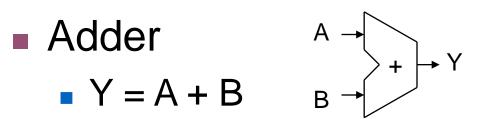

Arithmetic/Logic Unit

•
$$Y = F(A, B)$$

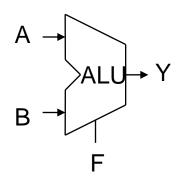

Building Blocks for 1 Bit ALU



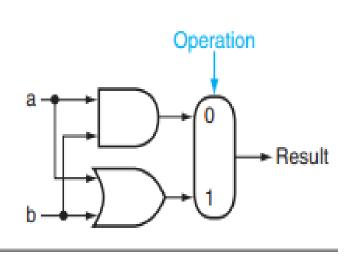


FIGURE B.5.1 The 1-bit logical unit for AND and OR.

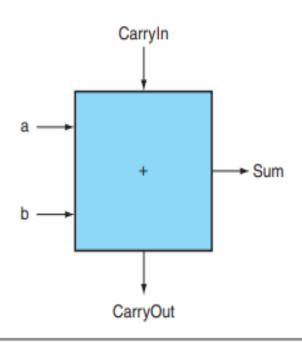


FIGURE B.5.2 A **1-bit adder.** This adder is called a full adder; it is also called a (3,2) adder because it has 3 inputs and 2 outputs. An adder with only the a and b inputs is called a (2,2) adder or half-adder.

Carry Out and simple 1 Bit ALU



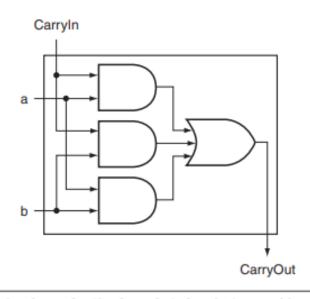


FIGURE B.5.5 Adder hardware for the CarryOut signal. The rest of the adder hardware is the logic for the Sum output given in the equation on this page.

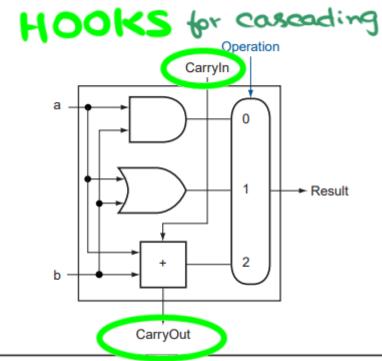


FIGURE B.5.6 A 1-bit ALU that performs AND, OR, and addition (see Figure B.5.5).

Building Blocks for 1 Bit Adder and some logic



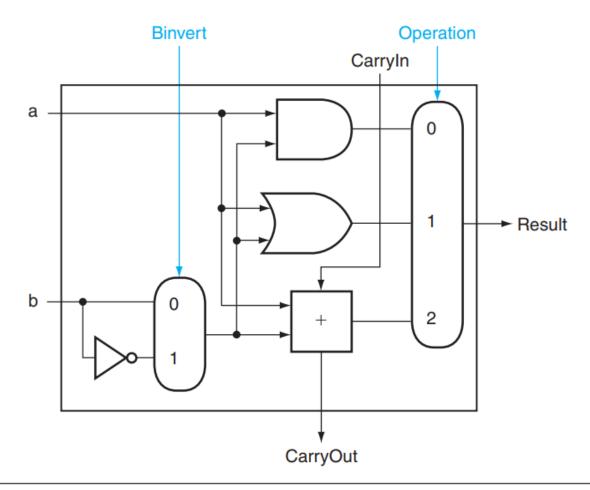


FIGURE B.5.8 A 1-bit ALU that performs AND, OR, and addition on a and b or a and $\overline{\mathbf{b}}$. By selecting $\overline{\mathbf{b}}$ (Binvert = 1) and setting CarryIn to 1 in the least significant bit of the ALU, we get two's complement subtraction of b from a instead of addition of b to a.

Simple 1 Bit ALU




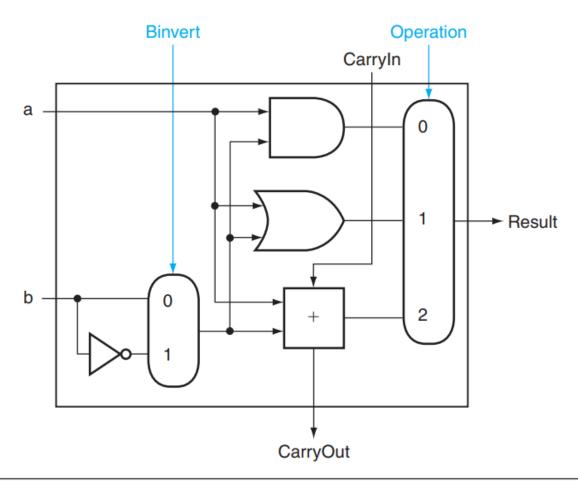


FIGURE B.5.8 A 1-bit ALU that performs AND, OR, and addition on a and b or a and $\overline{\mathbf{b}}$. By selecting $\overline{\mathbf{b}}$ (Binvert = 1) and setting CarryIn to 1 in the least significant bit of the ALU, we get two's complement subtraction of b from a instead of addition of b to a.

Developing Adder and Subtractor

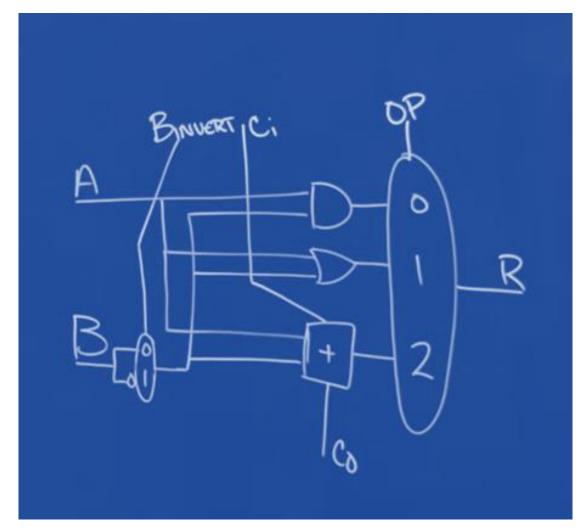

AND OR ADD SUB



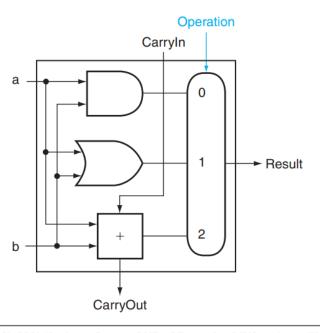


FIGURE B.5.6 A 1-bit ALU that performs AND, OR, and addition (see Figure B.5.5).

Nor and Nand Instructions



A MIPS ALU also needs a NOR function. Instead of adding a separate gate for NOR, we can reuse much of the hardware already in the ALU, like we did for subtract. The insight comes from the following truth about NOR:

De Morgan's theorem

$$(\overline{a+b}) = \overline{a} \cdot \overline{b}$$

That is, NOT (a OR b) is equivalent to NOT a AND NOT b. This fact is called DeMorgan's theorem and is explored in the exercises in more depth.

Since we have AND and NOT b, we only need to add NOT a to the ALU. Figure B.5.9 shows that change.

$$\begin{array}{ccc}
Q & \longrightarrow & R & = & Q & \longrightarrow & R \\
R & = & \overline{A + b} & R & = & \overline{A \cdot b}
\end{array}$$

$$\begin{array}{cccc}
R & \longrightarrow & & & & & & \\
R & \longrightarrow & & & & & \\
N & & & & & & & \\
N & \\
N & \\$$

$$\begin{array}{c}
a \rightarrow B = B \\
B = a \cdot B
\end{array}$$

$$\begin{array}{c}
R = a \cdot B \\
R = a \cdot B
\end{array}$$

$$\begin{array}{c}
A \times A \times D \\
A \times A \times D
\end{array}$$


NAND and NOR added to 1 bit ALU



AND OR ADD

SUB

NAND NOR

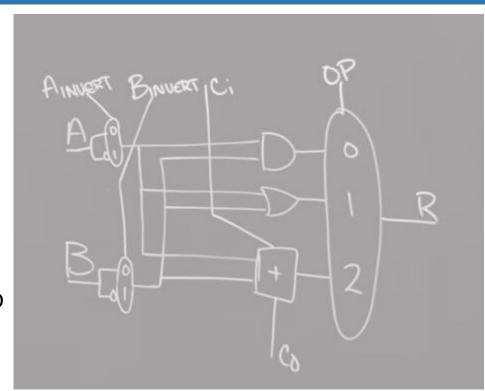

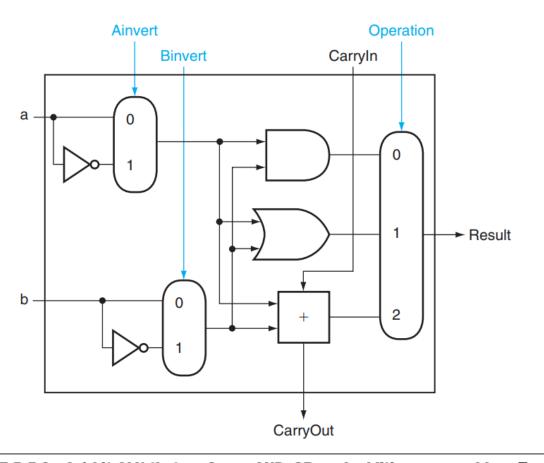


FIGURE B.5.9 A 1-bit ALU that performs AND, OR, and addition on a and b or \overline{a} and \overline{b} . By selecting \overline{a} (Ainvert = 1) and \overline{b} (Binvert = 1), we get a NOR b instead of a AND b.

1 Bit ALU with Overflow



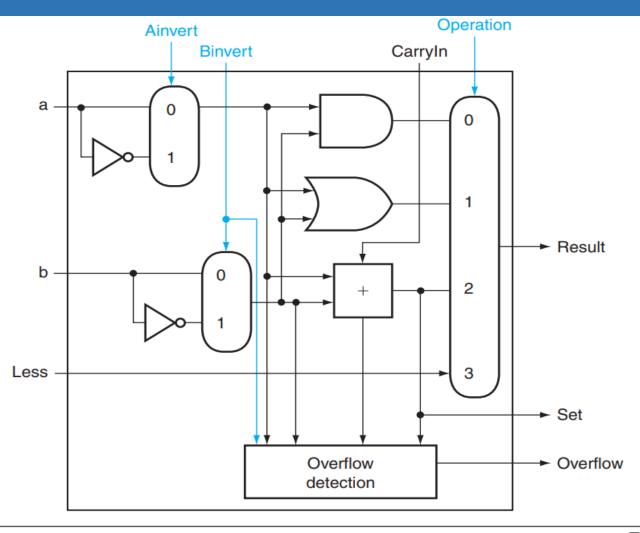


FIGURE B.5.10 (Top) A 1-bit ALU that performs AND, OR, and addition on a and b or \overline{b} , and (bottom) a 1-bit ALU for the most significant bit. The top drawing includes a direct input that is connected to perform the set on less than operation (see Figure B.5.11); the bottom has a direct output from the adder for the less than comparison called Set. (See Exercise B.24 at the end of this appendix to see how to calculate overflow with fewer inputs.)

Symbol of 1 Bit ALU



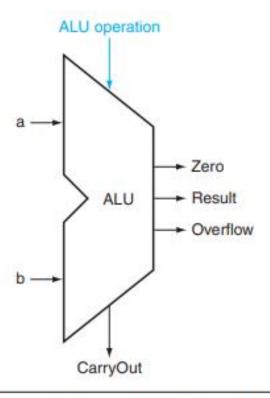


FIGURE B.5.14 The symbol commonly used to represent an ALU, as shown in Figure B.5.12. This symbol is also used to represent an adder, so it is normally labeled either with ALU or Adder.

32 Bit Adder and Carry Chain




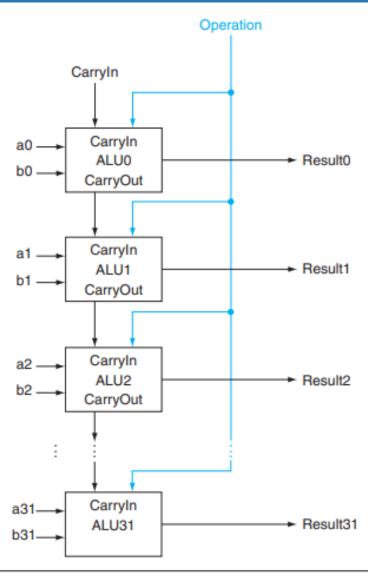


FIGURE B.5.7 A 32-bit ALU constructed from 32 1-bit ALUs. CarryOut of the less significant bit is connected to the CarryIn of the more significant bit. This organization is called ripple carry.

Repeat 32 ALU to make a 32 Bit ALU

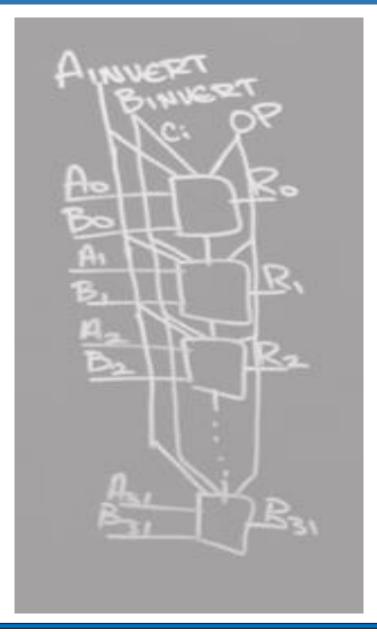




Adding Compare Instructions



Detect Zero

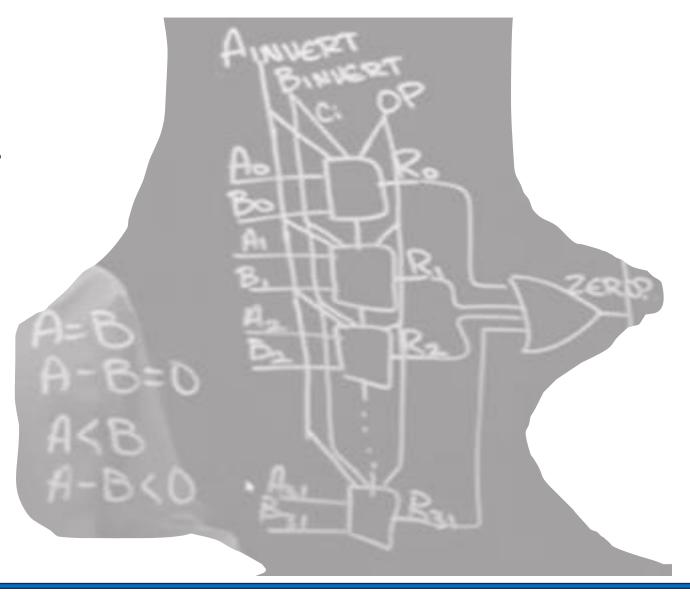Use Adder and Subtractor To Determine Sign of MSB. This gives indication of what number is bigger



'Less' than Instruction




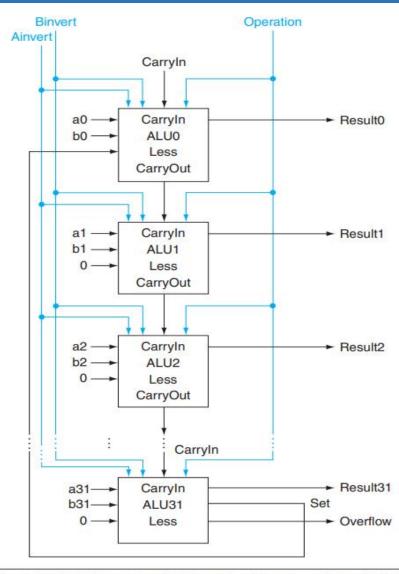


FIGURE B.5.11 A 32-bit ALU constructed from the 31 copies of the 1-bit ALU in the top of Figure B.5.10 and one 1-bit ALU in the bottom of that figure. The Less inputs are connected to 0 except for the least significant bit, which is connected to the Set output of the most significant bit. If the ALU performs a - b and we select the input 3 in the multiplexor in Figure B.5.10, then Result = 0 ... 001 if a < b, and Result = 0 ... 000 otherwise.

Final ALU

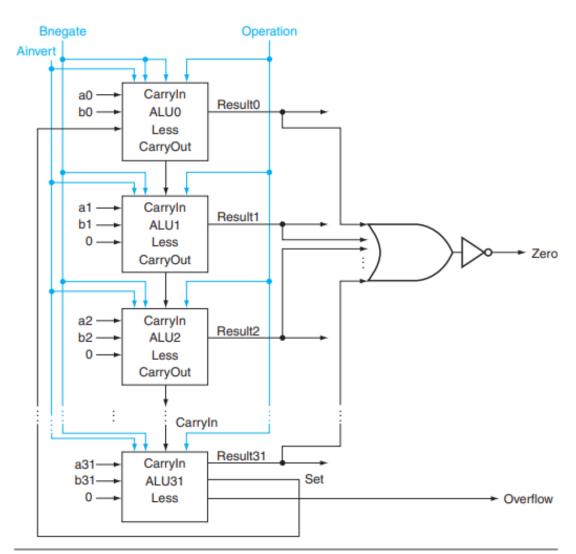



ALU control lines	Function		
0000	AND		
0001	OR		
0010	add		
0110	subtract		
0111	set on less than		
1100	NOR		

 ${\bf FIGURE~B.5.13~The~values~of~the~three~ALU~control~lines,~Bnegate,~and~Operation,~and~the~corresponding~ALU~operations.}$

FIGURE B.5.12 The final 32-bit ALU. This adds a Zero detector to Figure B.5.11.


Zero detector Instruction



```
Zero = (Result31 + Result30 + ... + Result2 + Result1 + Result0)
```


Figure B.5.12 shows the revised 32-bit ALU. We can think of the combination of the 1-bit Ainvert line, the 1-bit Binvert line, and the 2-bit Operation lines as 4-bit control lines for the ALU, telling it to perform add, subtract, AND, OR, or set on less than. Figure B.5.13 shows the ALU control lines and the corresponding ALU operation.

Less 0

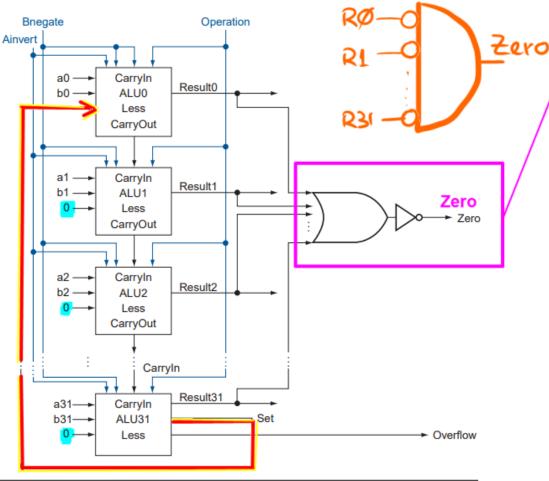

Showing Overflow and Set circuit



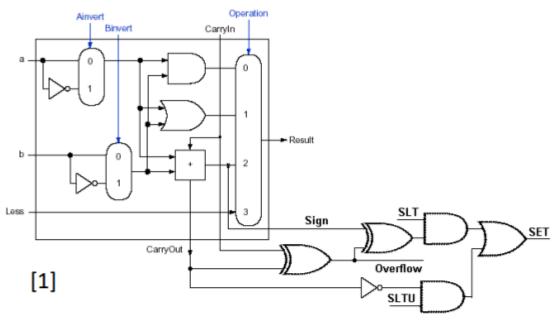

1-bit ALU for the MSB bit with overflow detection and set generation


32-bit ALU built with 32 x 1-bit ALUs

Less[31:1] = 0, Less[0] = Set form ALU31

Subtraction operations: CarryIn=Binvert = 1


Addition or logical operations: CarryIn=Binvert = 0

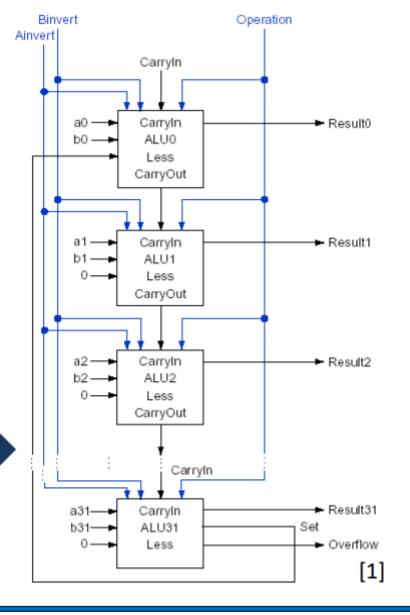We can simplify the control: CarryIn = Binvert = Bnegate



Data path and Control path in a CPU



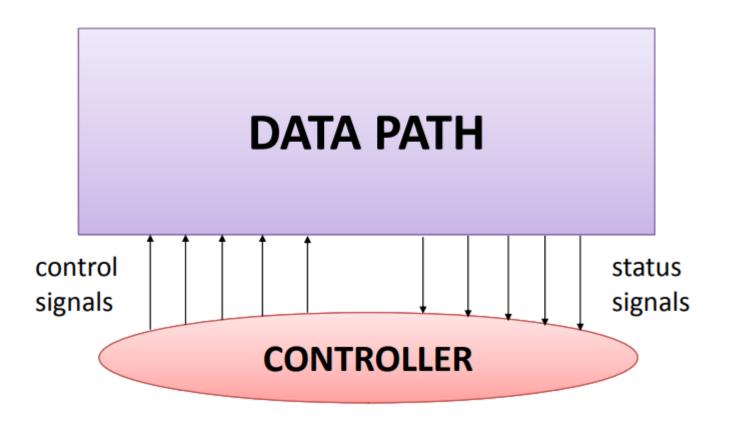


Building a Datapath



- Datapath
 - Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
 - Refining the overview design

Instruction Fetch



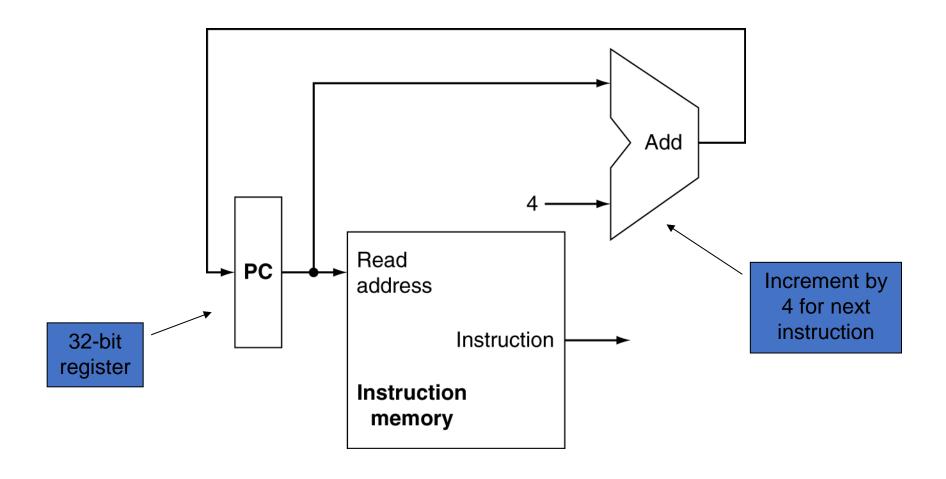

Load / Store / Add / Sub / Logic / slt Instructions



- Look at Building Blocks of MIPS Implementation
- Study two MIPS implementations
 - A simplified version
 - A more realistic pipelined version
- Simple subset, shows most aspects
 - Memory reference: lw, sw
 - Arithmetic/logical: add, sub, and, or, slt
 - Control transfer: beq, j


Instruction Execution



- PC → instruction memory, fetch instruction
- Register numbers → register file, read registers
- Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
 - Access data memory for load/store
 - PC ← target address or PC + 4

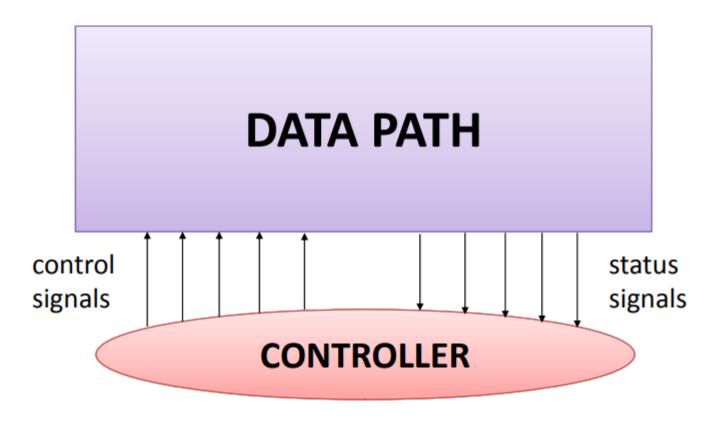CPU consists of Data path and Control path





Building a Datapath



- Datapath
 - Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
 - Refining the overview design


Components for Building MIPS CPU




- Register
- Adder
- ALU
- Multiplexer
- Register file
- Program memory
- Data memory
- Bit manipulation components



MIPS Components - Register

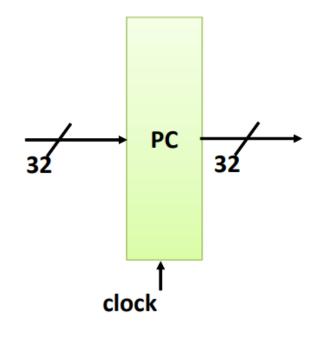


MIPS components - Multiplexers

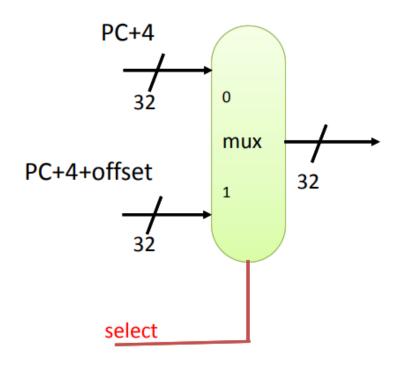




MIPS Components - Adder

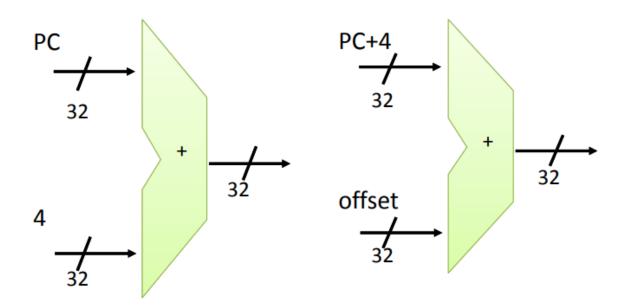

MIPS Components - ALU

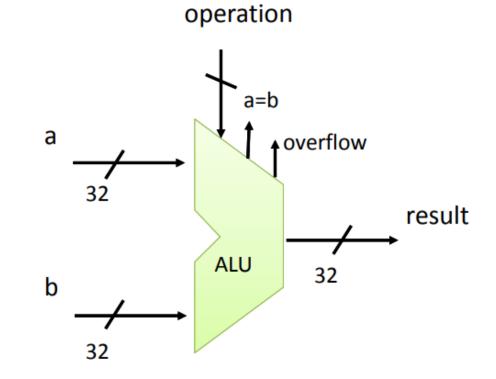




MIPS Components - register file


Register Number Read Reg 1 Read Data 1 Read Read Read Registers Write Reg Read Data 2 Reg Write Reg Write

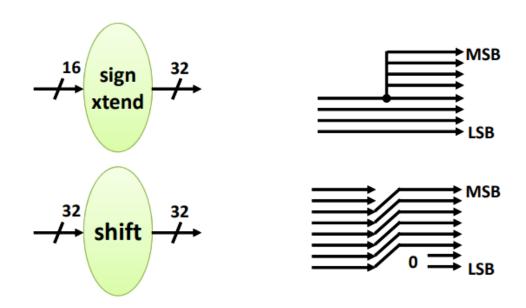MIPS Components -Bit manipulation circuits






MIPS Components - Data memory

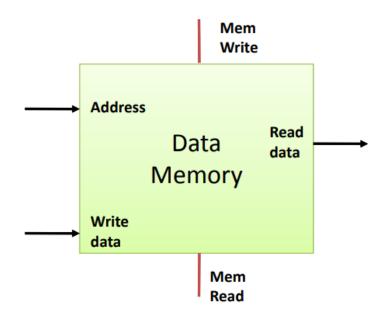

MIPS Components: Program memory

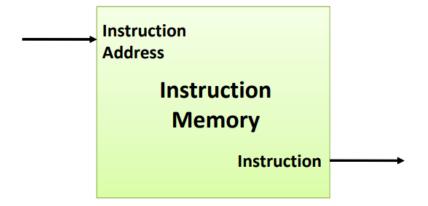

Build MIPS Data path – Step by Step



Build the datapath step by step as follows

- Start with R class instructions
- Include other instructions one by one
- Identify control signals
- Interconnect datapath and controller

Two Components for R format ALU




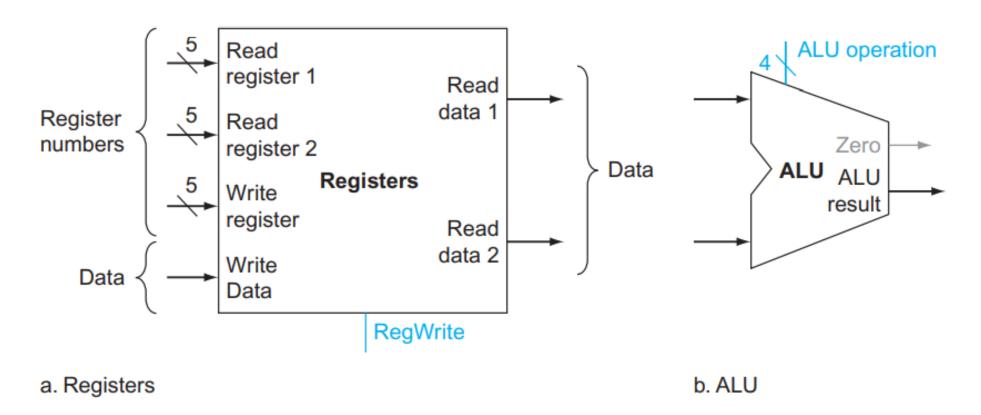


FIGURE 4.7 The two elements needed to implement R-format ALU operations are the register file and the ALU. The register file contains all the registers and has two read ports and one write port. The design of multiported register files is discussed in Section B.8 of Appendix B. The register file always outputs the contents of the registers corresponding to the Read register inputs on the outputs; no other control inputs are needed. In contrast, a register write must be explicitly indicated by asserting the write control signal. Remember that writes are edge-triggered, so that all the write inputs (i.e., the value to

R-Format Instructions

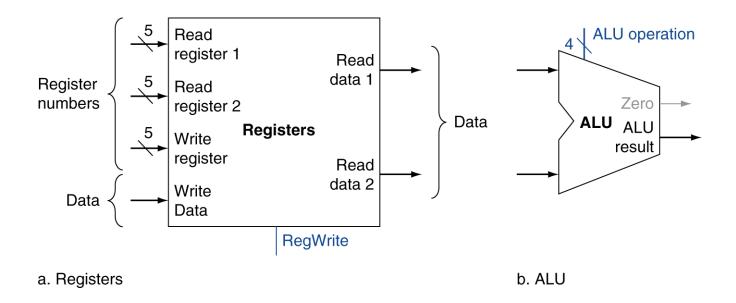

- Read two register operands
- Perform arithmetic/logical operation
- Write register result



MIPS Subset of R format to start implementation



- Arithmetic logic instructions
 - -add, sub, and, or, slt
- Memory reference instructions
 - -lw, sw
- Control flow instructions
 - beq, j

Develop Data path for add, sub, and, or, slt



- fetch instruction
- address the register file
- pass operands to ALU
- pass result to register file

increment PC

actions


required

Format: add \$t0, \$s1, \$s2

000000	10001	10010	01000	00000	100000
ор	rs	rt	rd	shamt	funct

Instruction Fetch




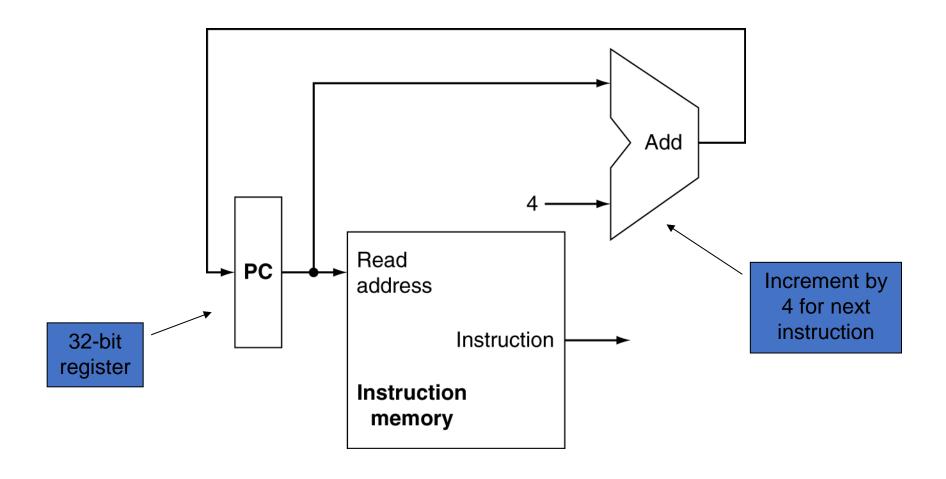


Basic CPU Operations - 1



Fetching Instruction

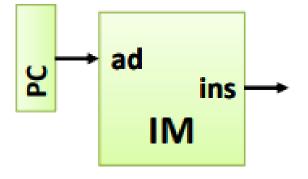


Addressing Register File

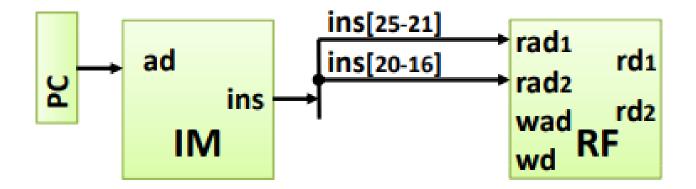


Basic CPU Operations - 2



Passing the Result to Register File

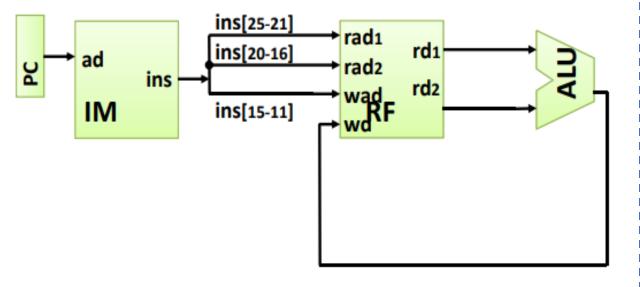


Passing Operands to ALU

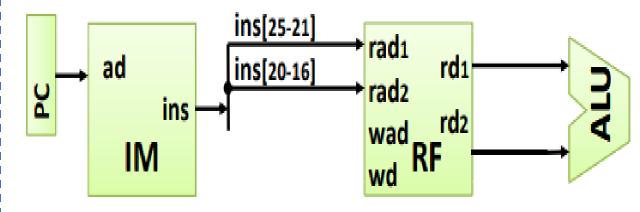

Basic CPU Operations - 3




Incrementing PC

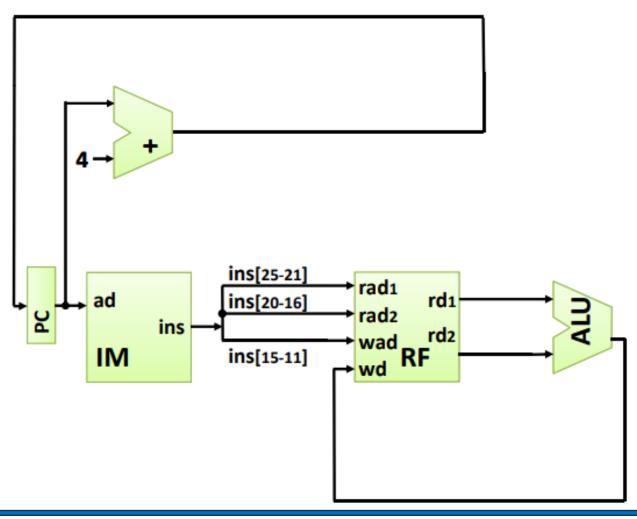

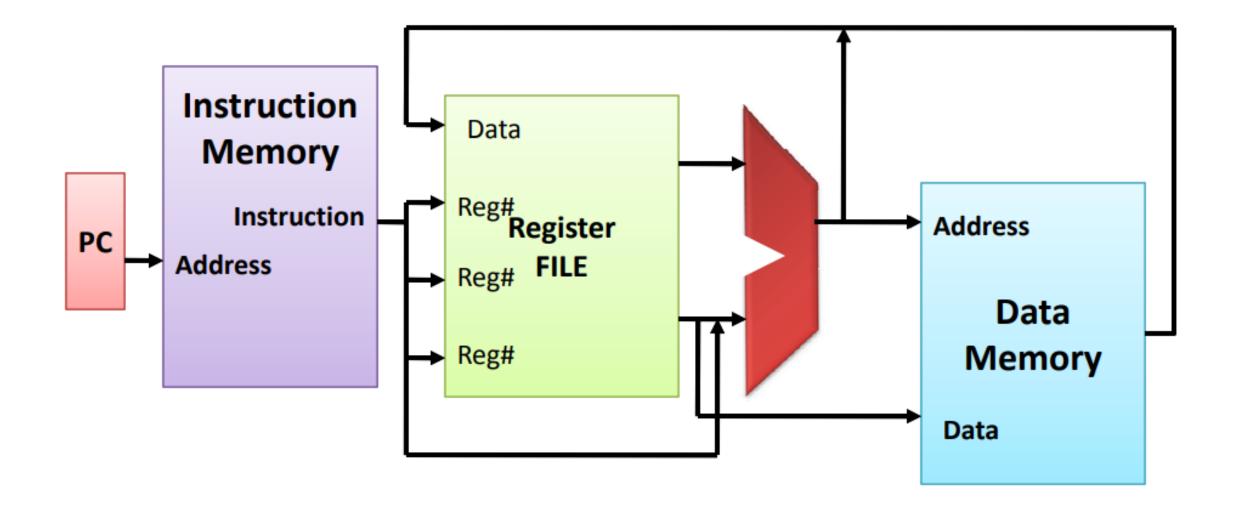Overview of Simple CPU Design for R Format





Readings



- Chap 4 of P&H Textbook
- Appendix B of P&H Textbook